

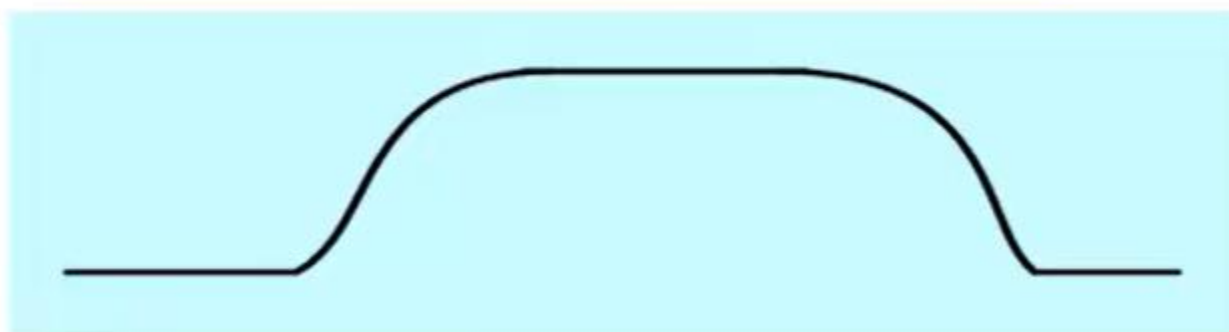


Transient Response

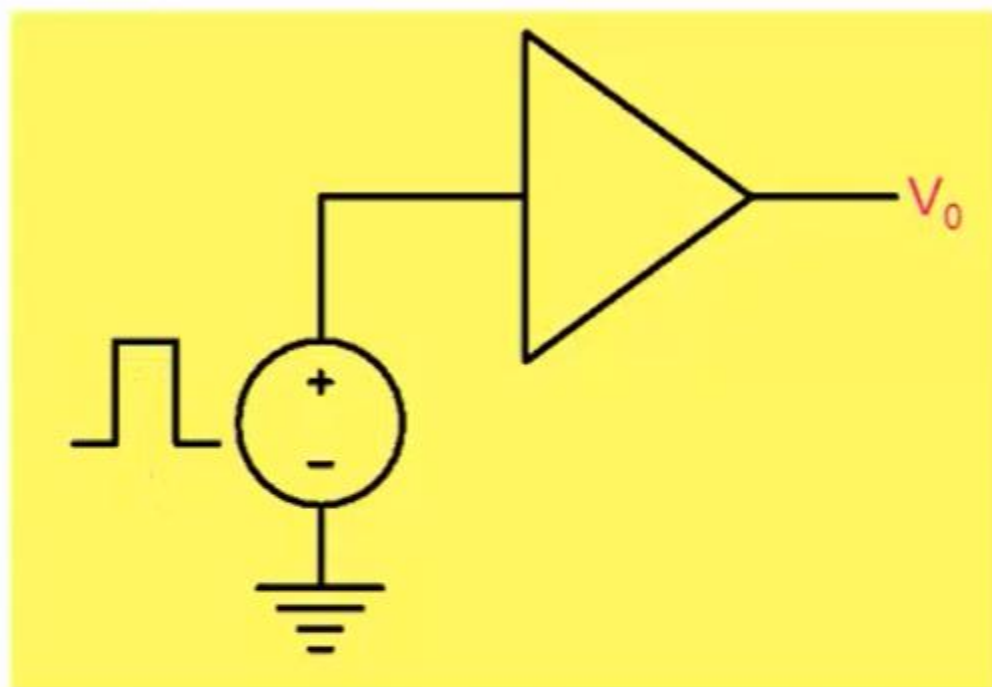



Rise time and fall time


Overshoot and time Settling time

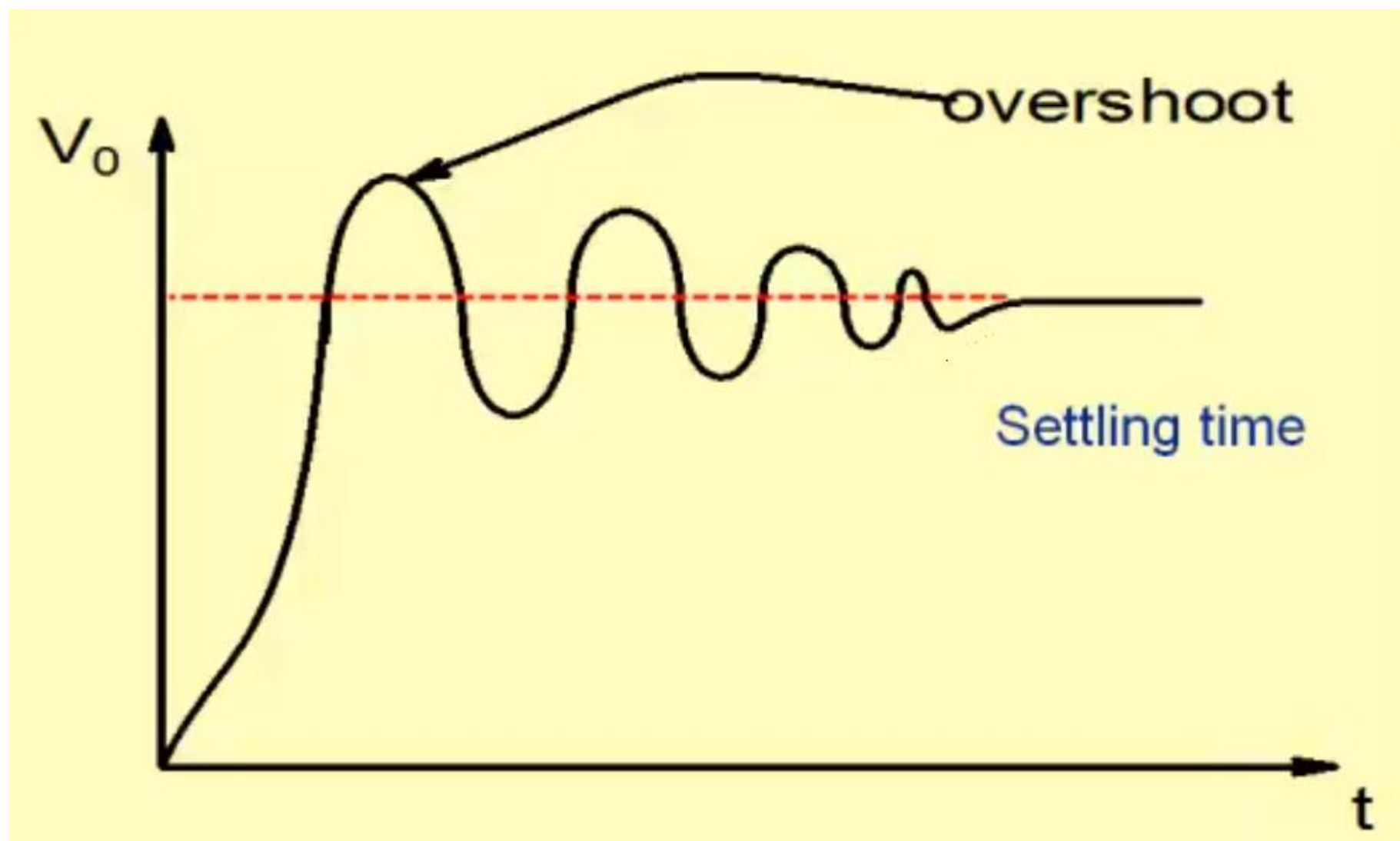

Distortion:

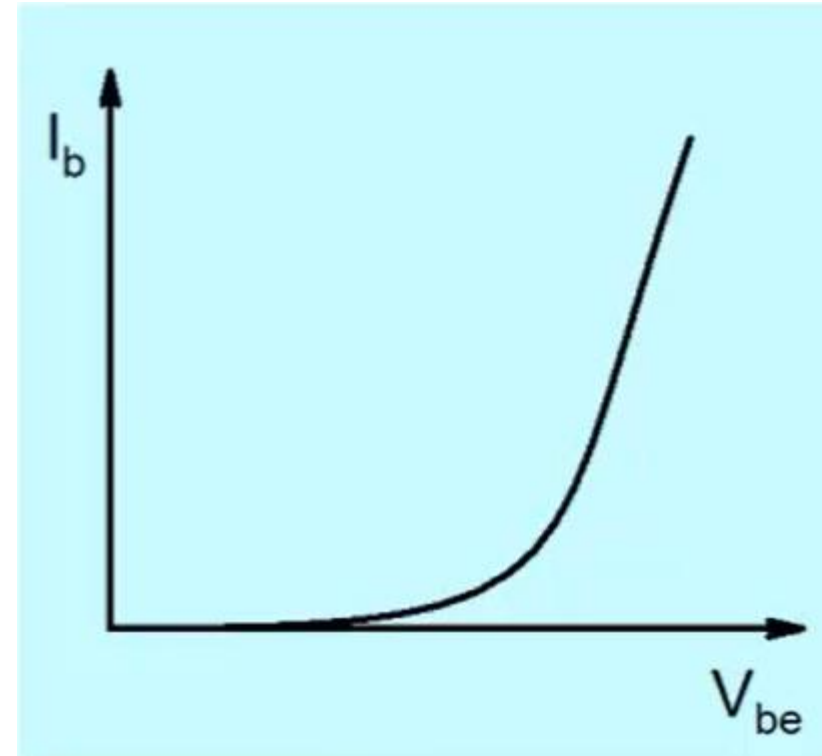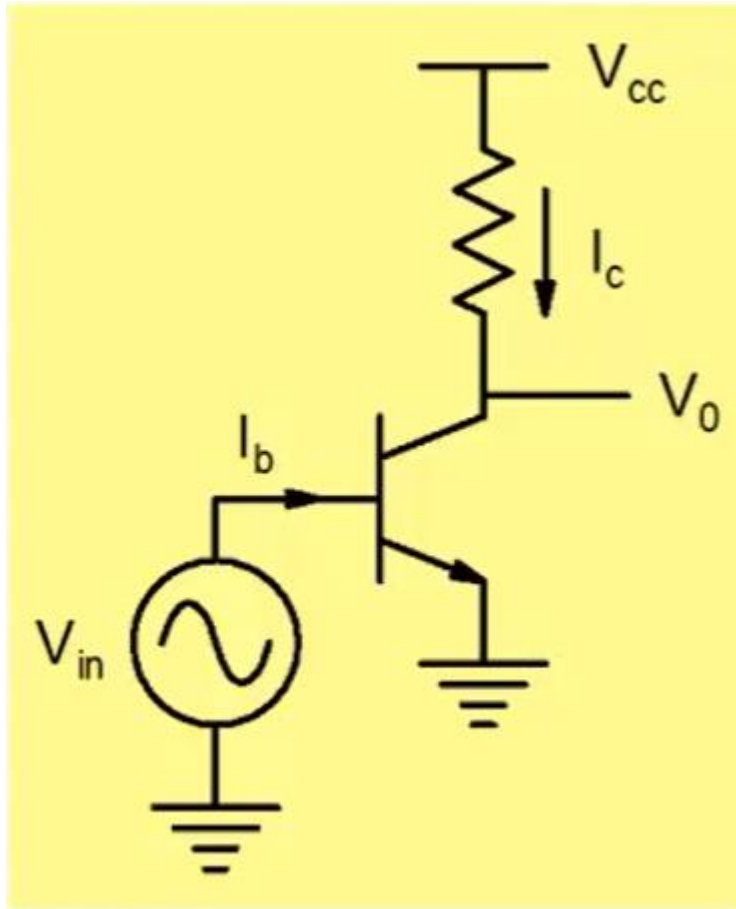All amplifiers are nonlinear because transistors used for building amplifier are nonlinear elements.



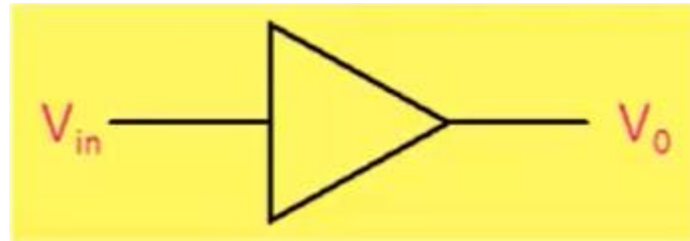

$$V_{in} = a_0 \sin \omega t$$

$$V_o = b_0 + b_1 \sin \omega t + b_2 \sin 2\omega t + b_3 \sin 3\omega t + \dots$$

$$HD_2 = \frac{b_2}{b_1} \times 100$$

$$HD_3 = \frac{b_3}{b_1} \times 100$$

$$THD = \frac{\sqrt{b_2^2 + b_3^2 + \dots}}{b_1} \times 100$$

Example

$$V_0 = kV_{in} + \frac{k}{10}V_{in}^2$$


$$V_{in} = a_0 \sin \omega t$$




$$V_0 = \frac{ka_0^2}{20} + ka_0 \sin \omega t - \frac{ka_0^2}{20} \cos 2\omega t$$

$$THD = HD_2 = \frac{ka_0^2 / 20}{ka_0} \times 100 = 5a_0$$

Distortion increases with magnitude of input signal !

Maximum Voltage Swing


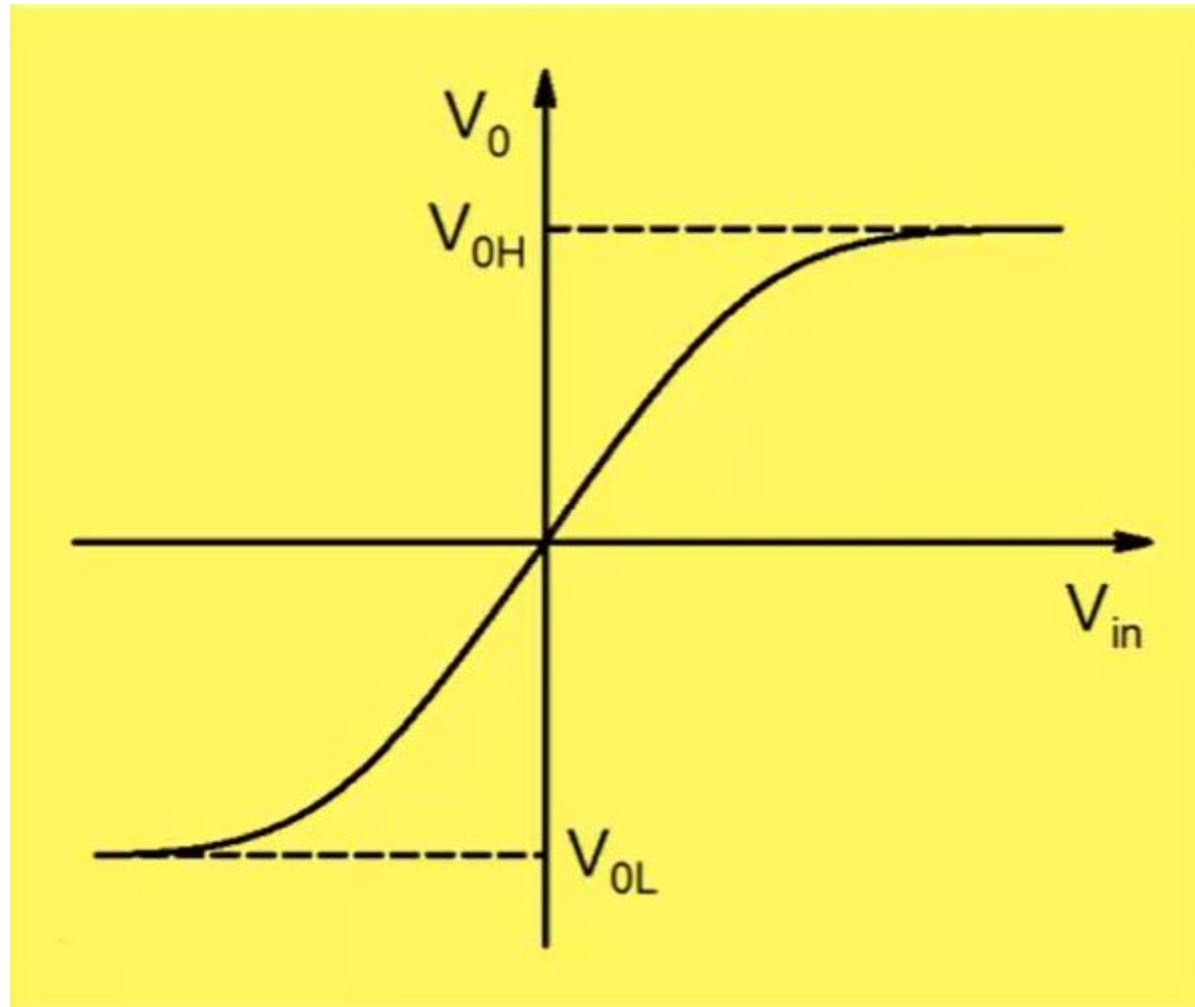


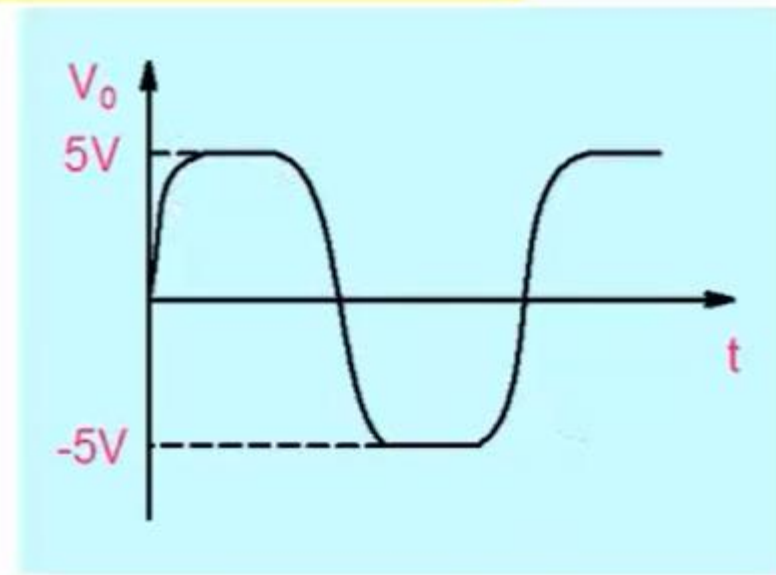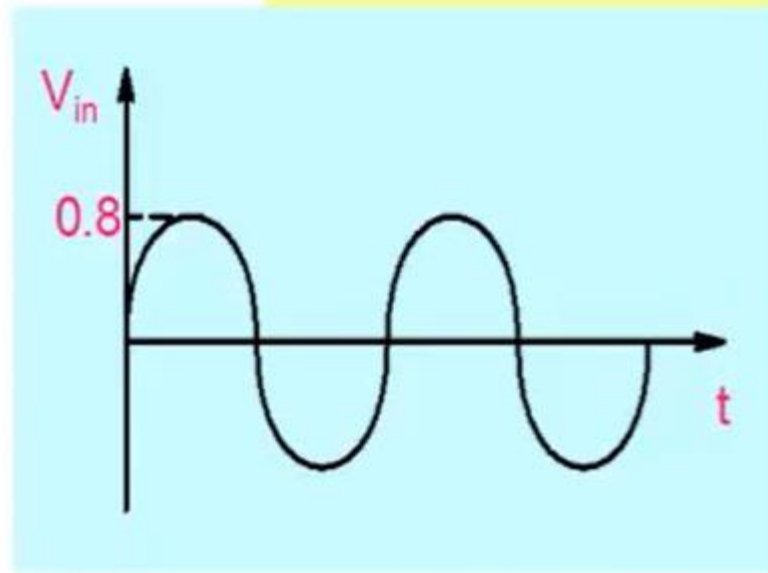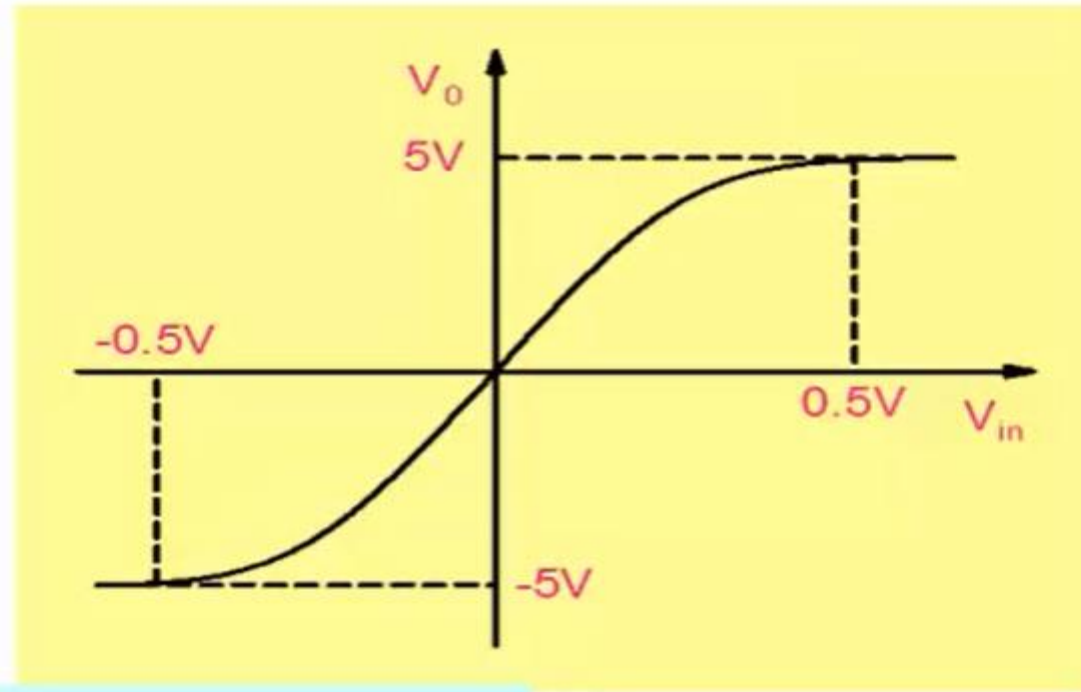


Rail-to-Rail output voltage swing

$$V_{OH} \leq V_{DD}$$




$$V_{OL} \geq V_{SS}$$

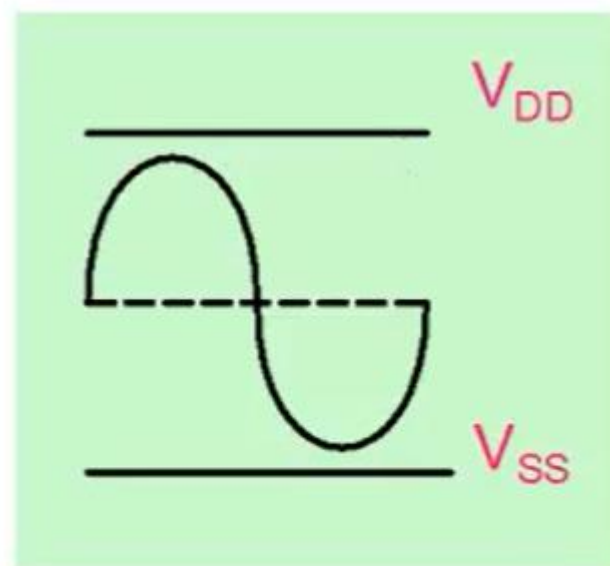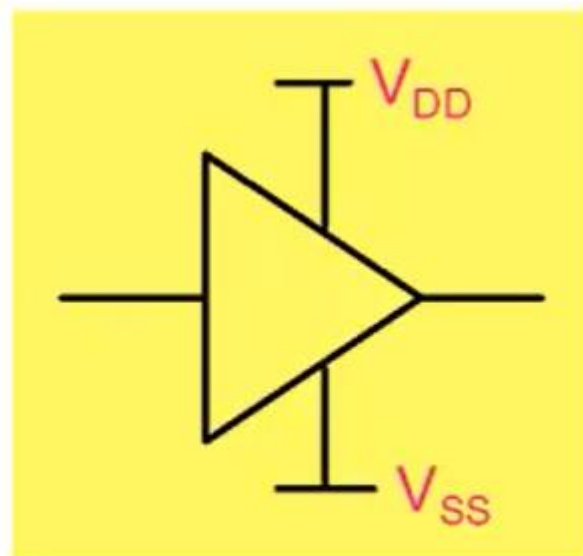

Effect of Load Resistance

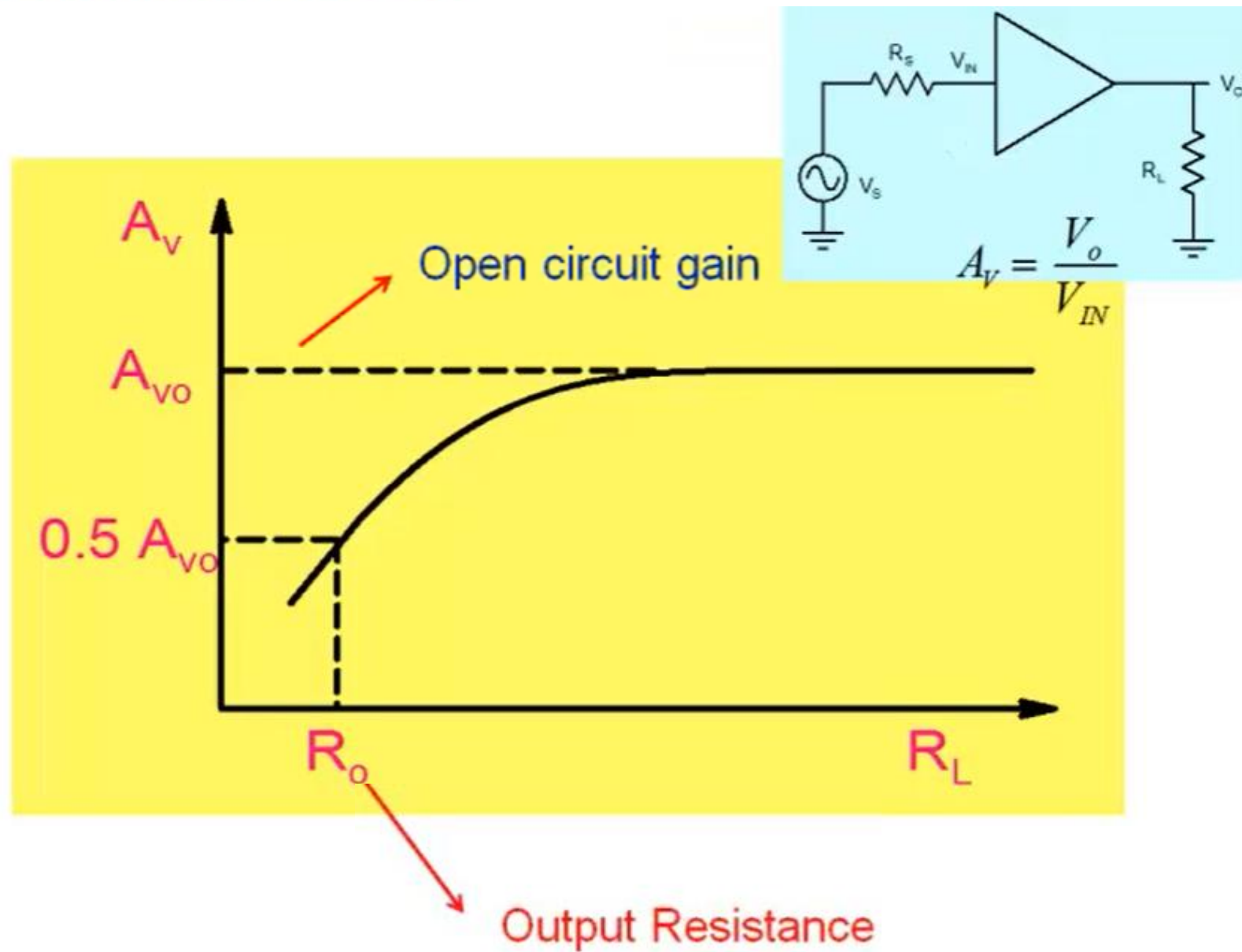


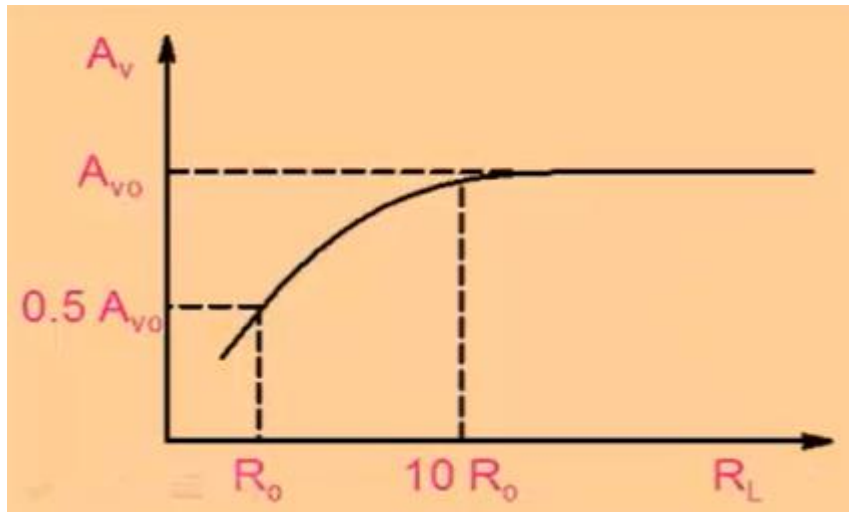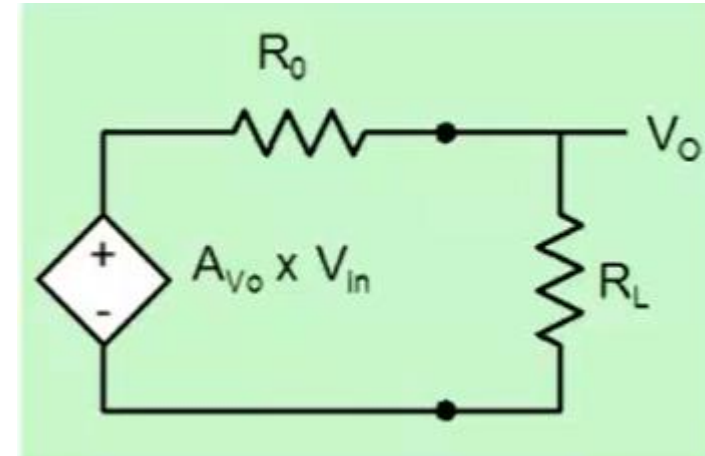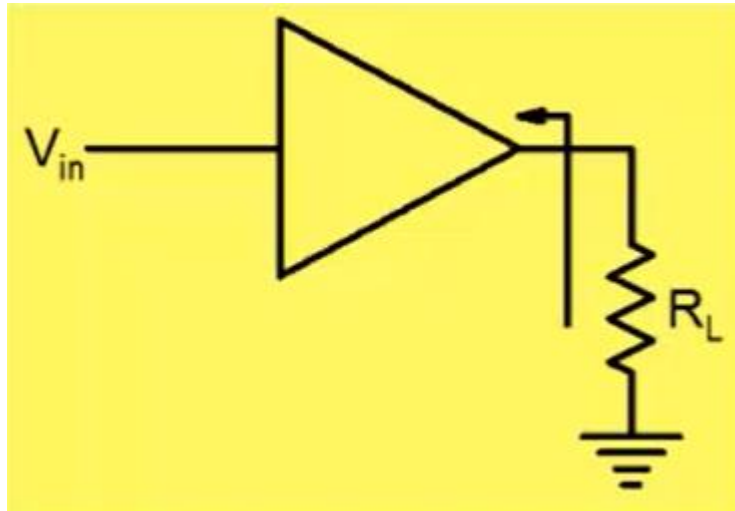Open circuit voltage gain and output resistance






$$V_o = A_{V0} \times V_{in} \left(\frac{R_L}{R_0 + R_L} \right)$$

Input Resistance

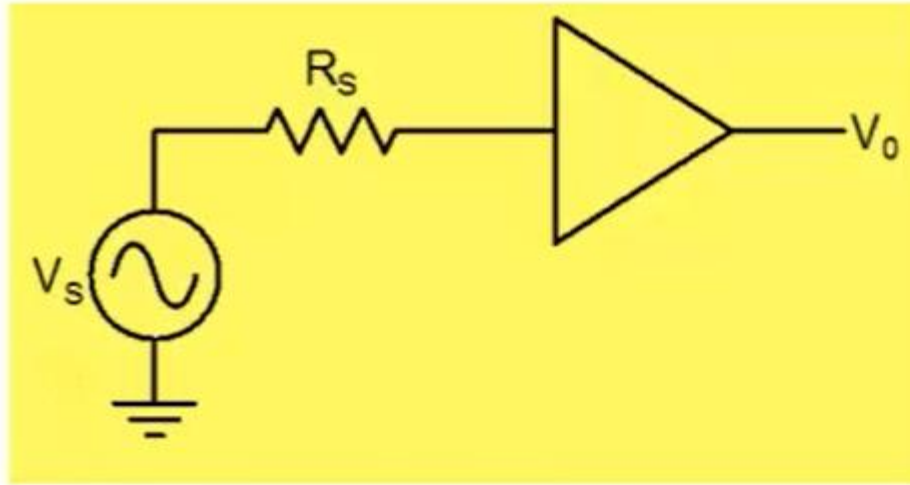




$$A_{VS} = \frac{V_o}{V_s}$$

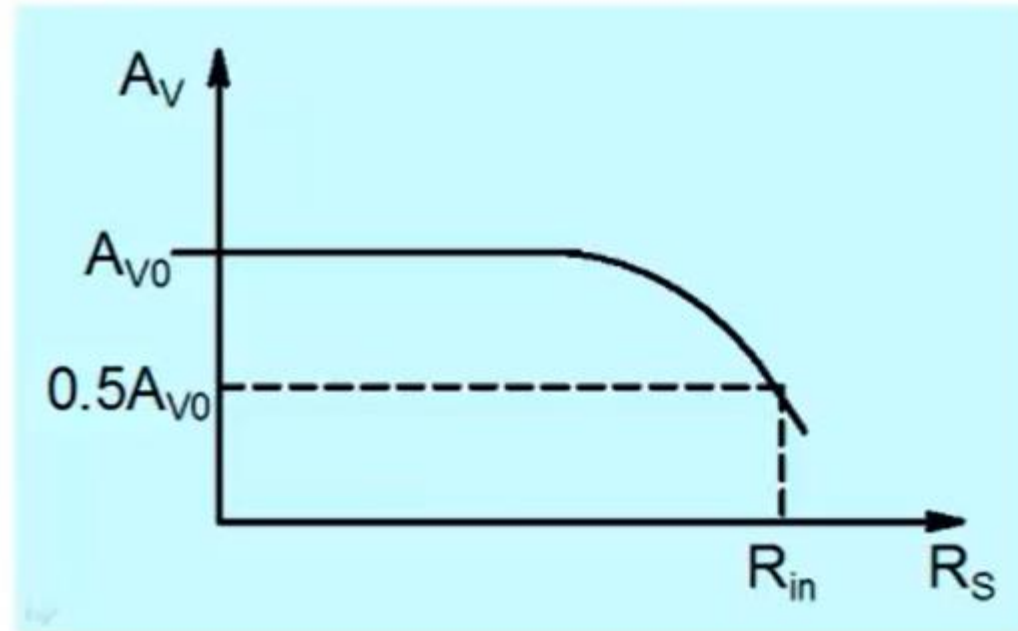


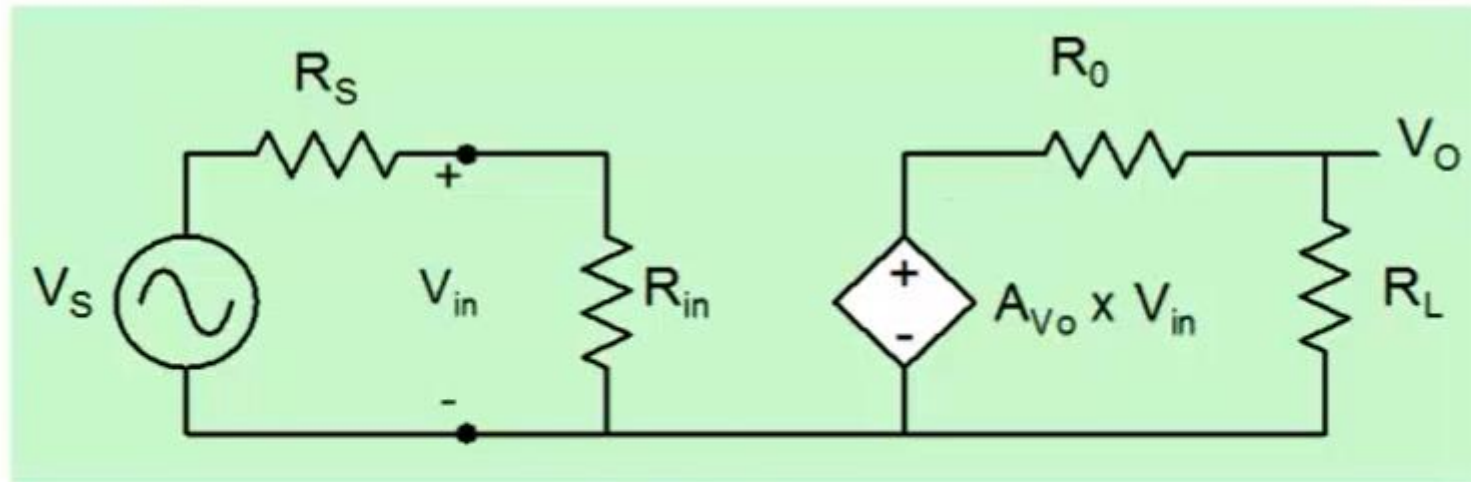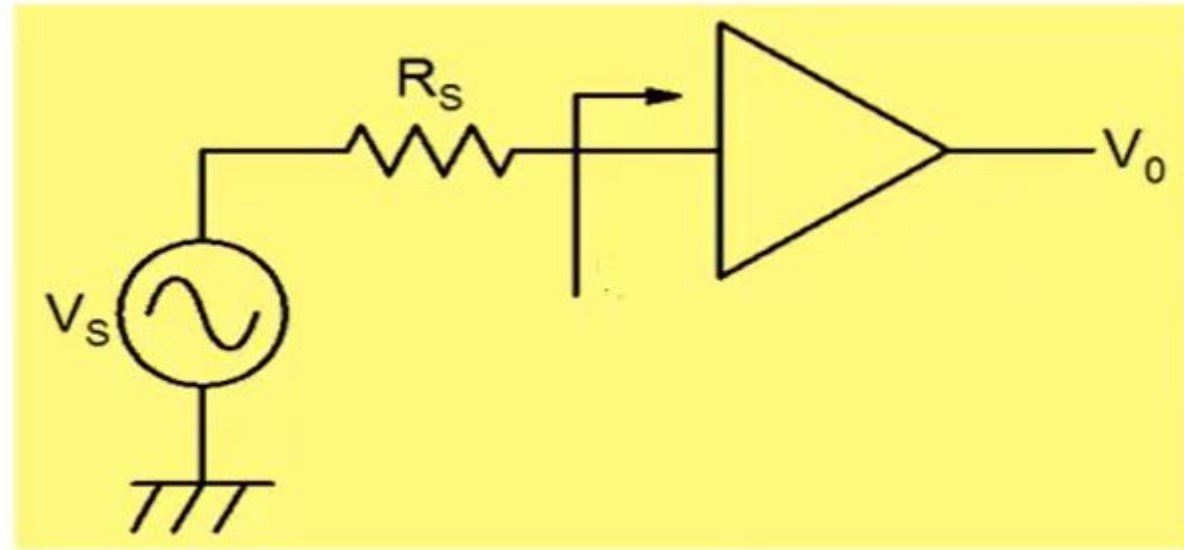

$$A_{VS} = A_{V_0} \times \frac{R_{in}}{R_S + R_{in}} \times \frac{R_L}{R_0 + R_L}$$

NOISE

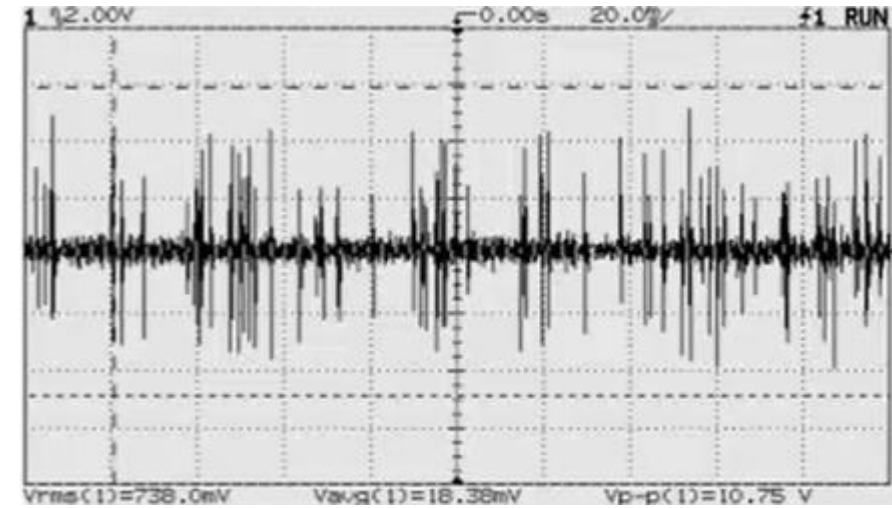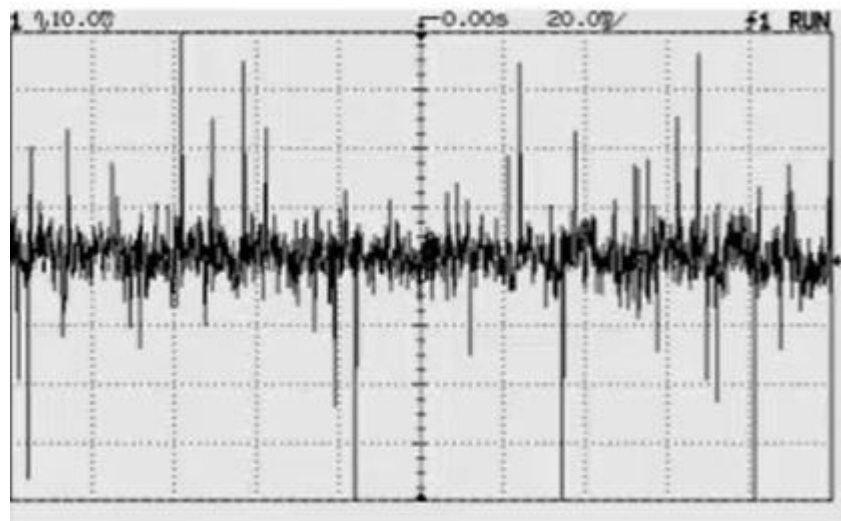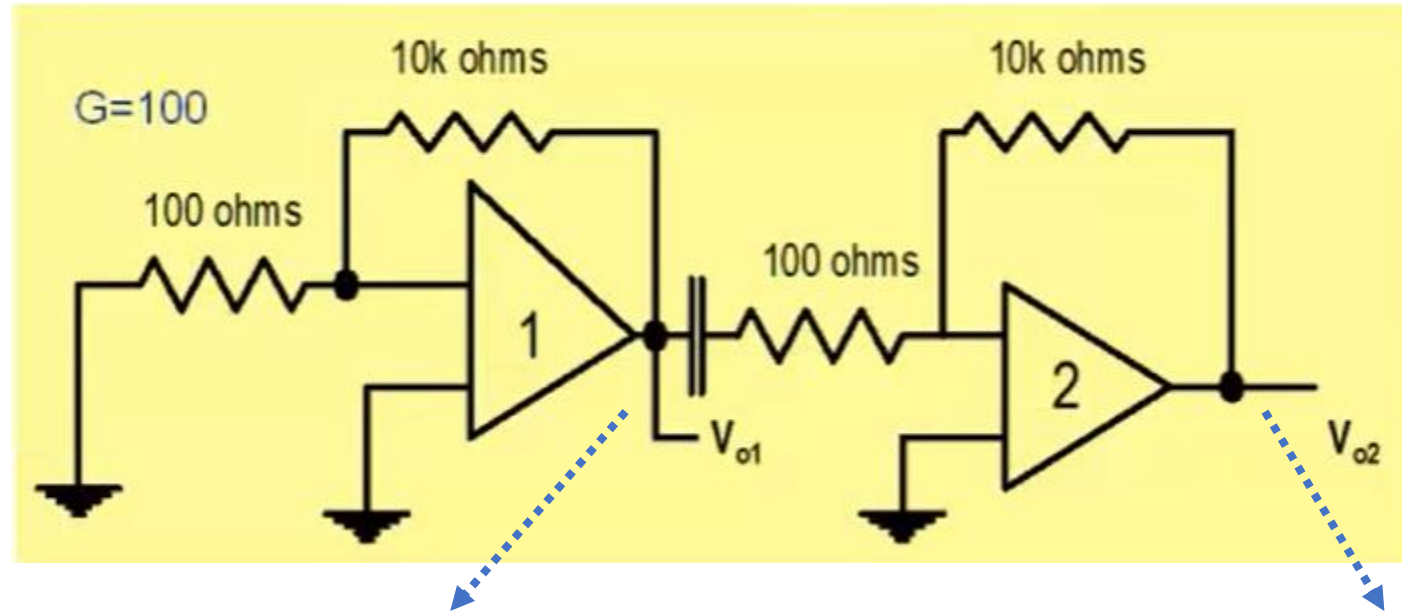

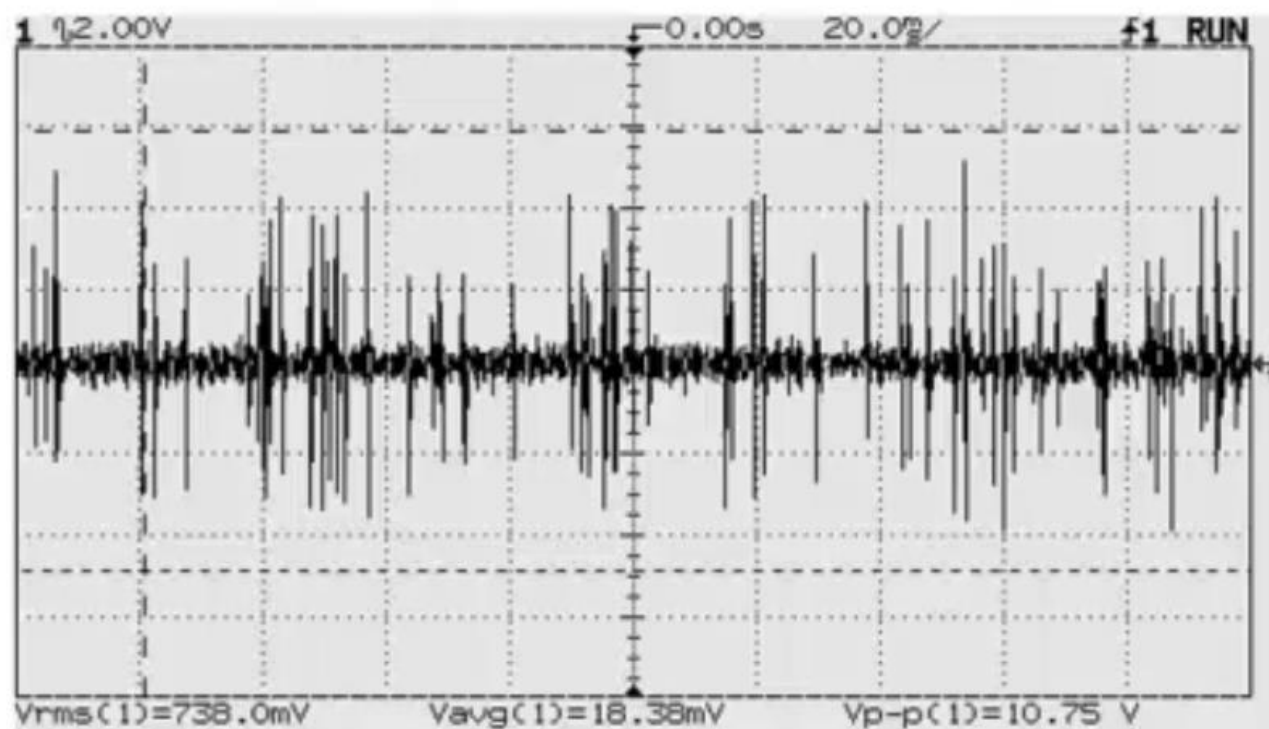


$$F = \frac{\text{Total Output Noise Power}}{\text{Output Noise due to Input Noise Only}}$$

$$F=1.26$$


$$\text{Noise Figure : } NF=10 \times \text{Log}_{10}(F)$$

$$NF=1 \text{ dB}$$


Maximum Current Driving Capability

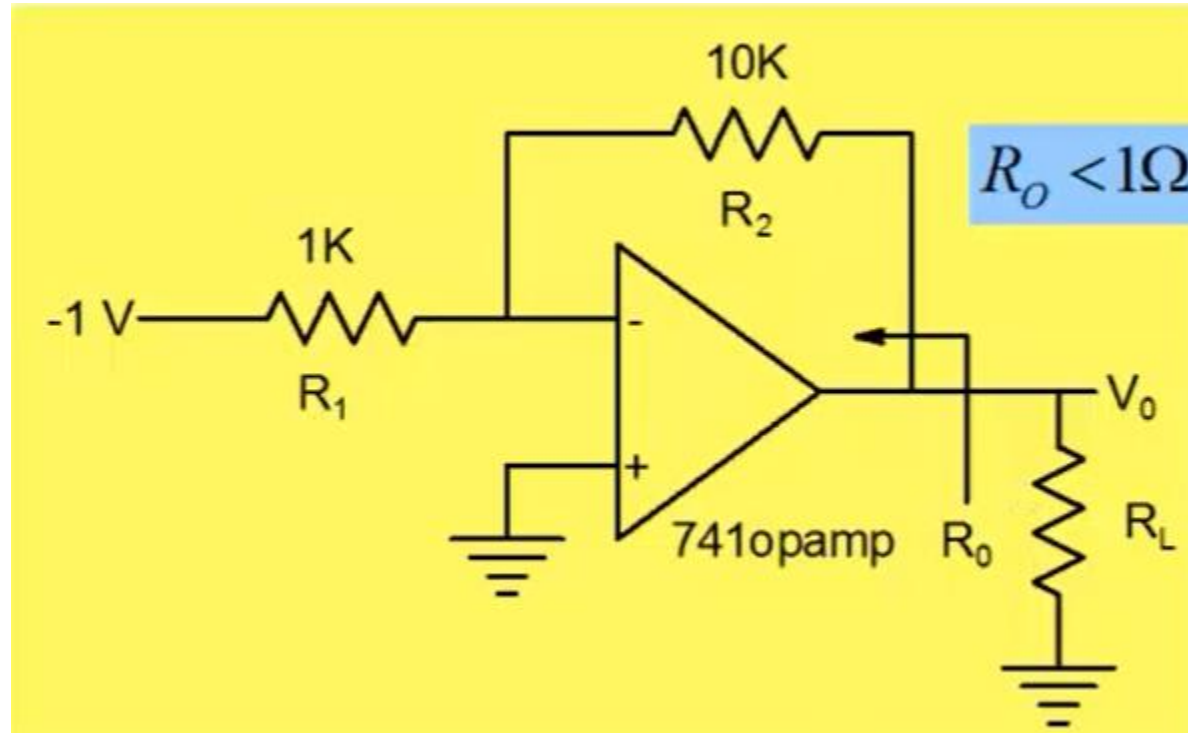


$$V_0 = -\frac{R_2}{R_1} V_{in} = 10V$$


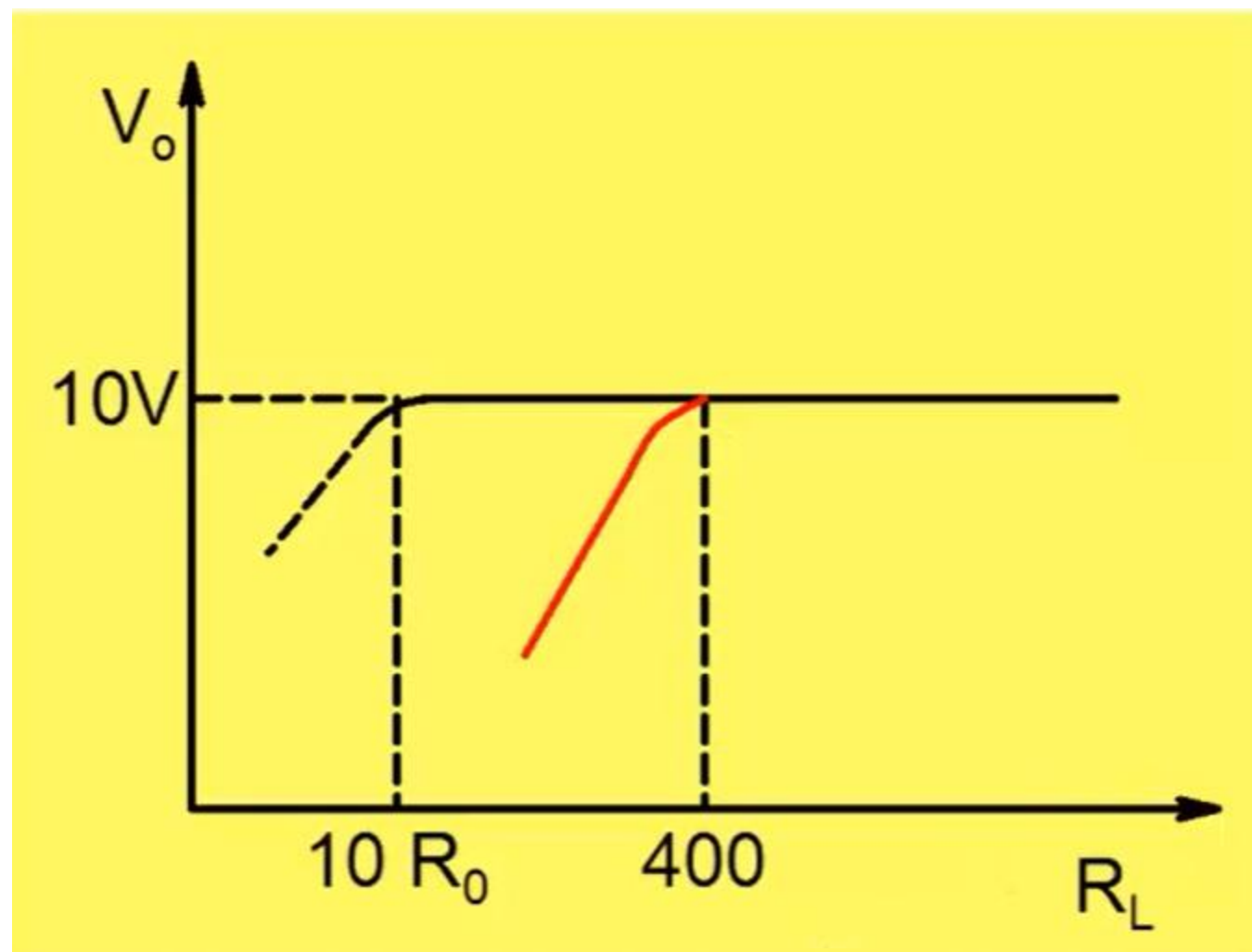


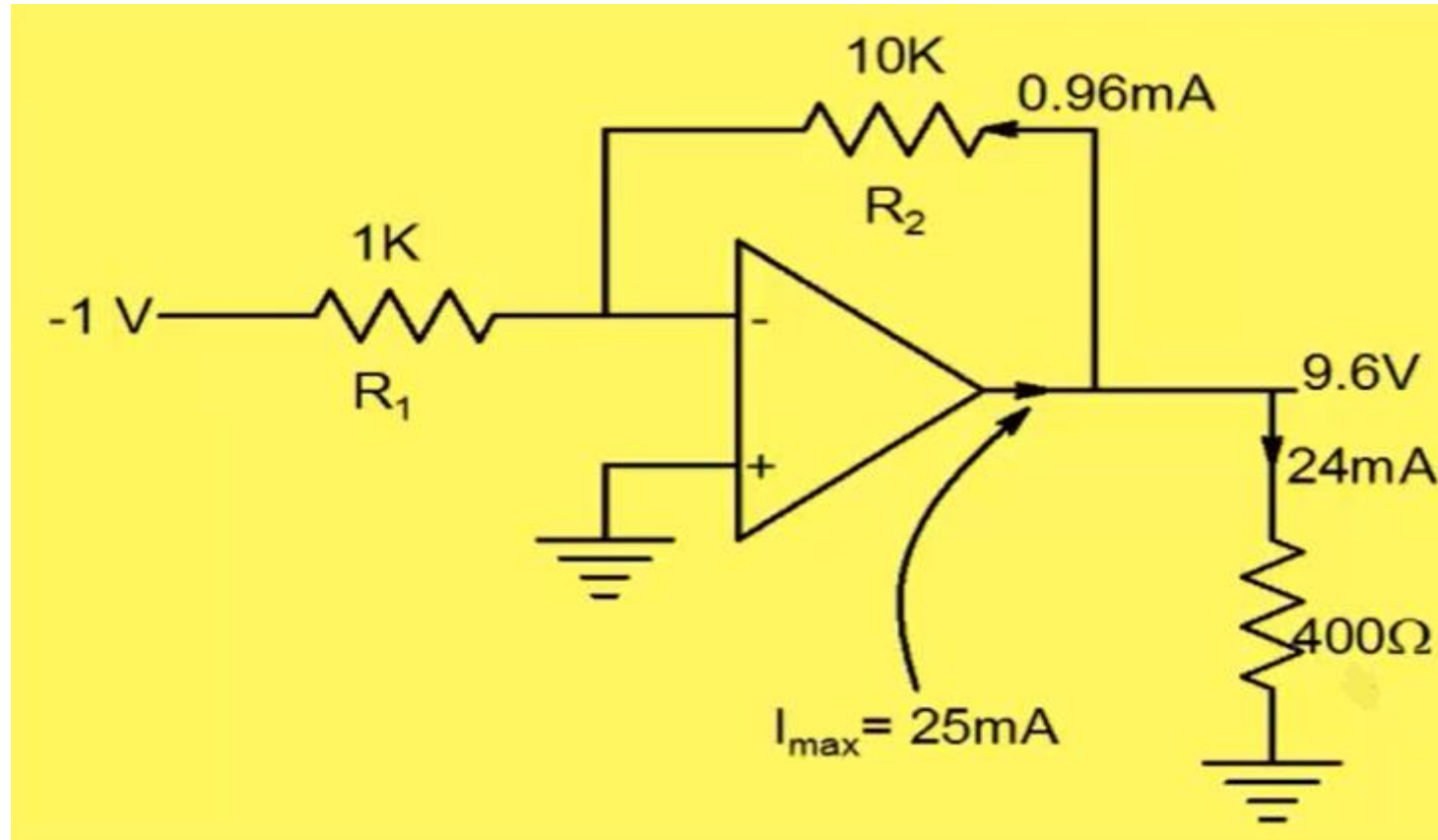Opamp has maximum current drive capability of 25mA



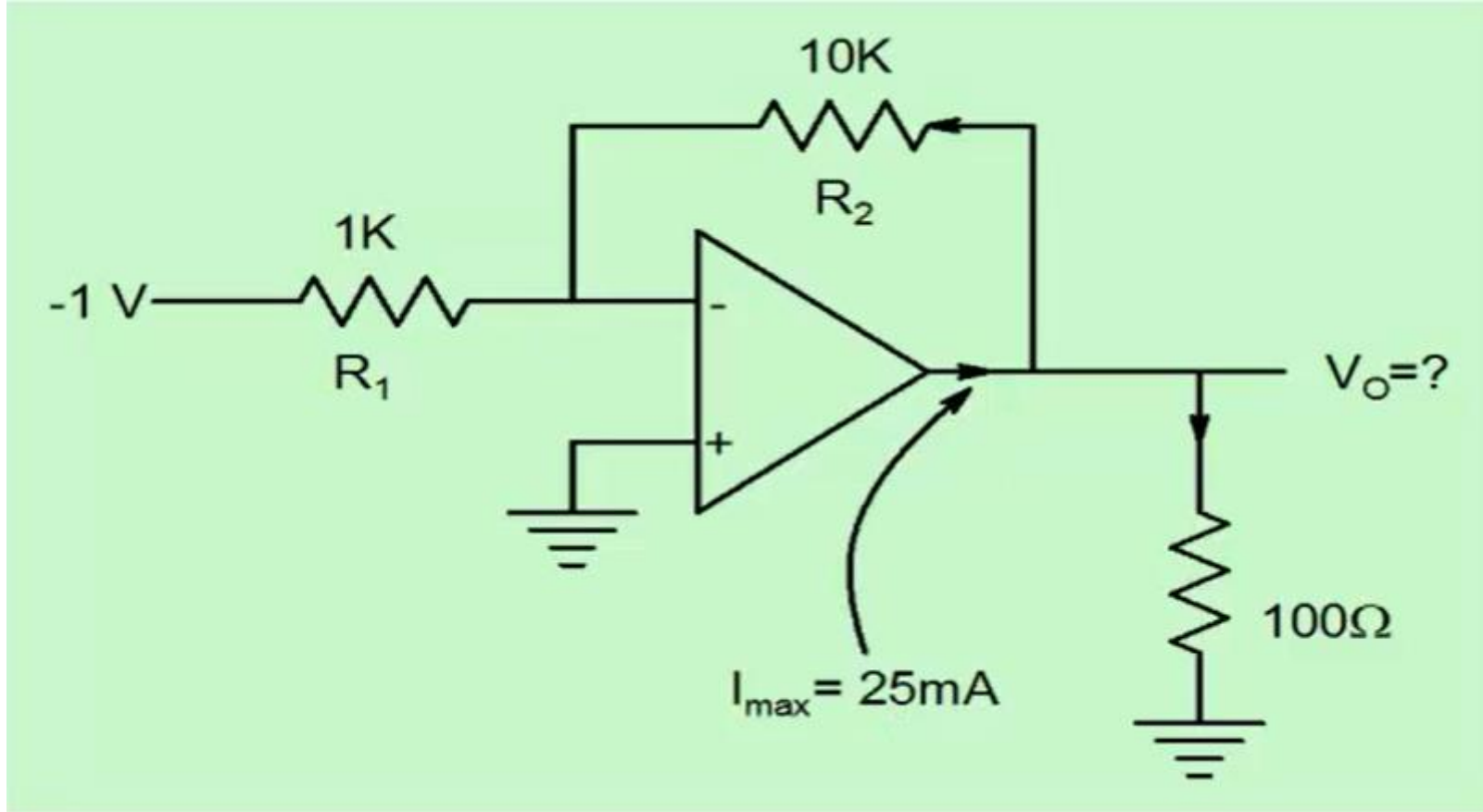


Slew rate

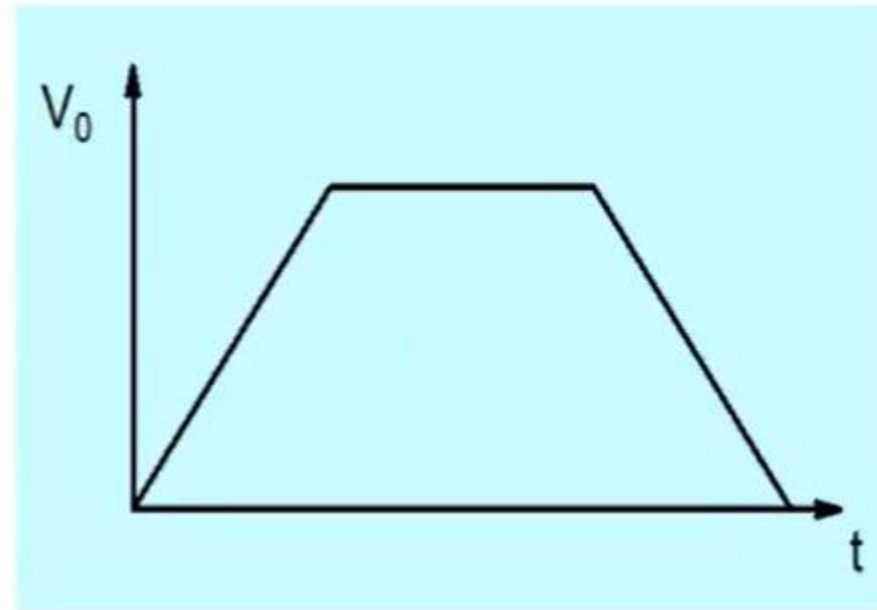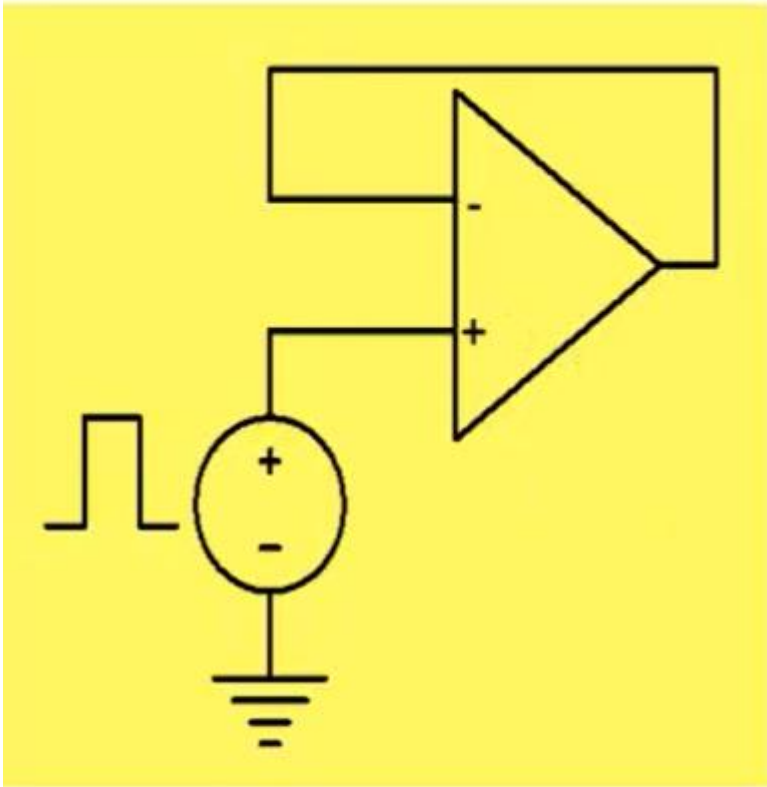

$$\text{Slew rate} = \left. \frac{dv_0}{dt} \right|_{\text{max}}$$

Other specifications

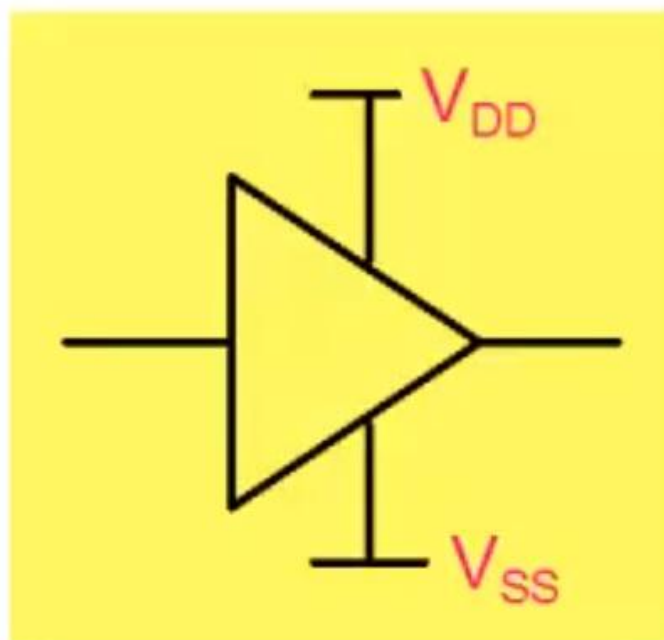

$$\eta = \frac{P_L}{P_{supply}}$$

Power supply rejection ratio, common mode rejection ratio.....


Summary

$$v_o = A_v(f, V_{in}, R_L, R_S, T) \times v_{in} + \tilde{e}_N$$

The diagram illustrates the relationship between the variables in the equation and specific circuit parameters. Red arrows point from each variable in the equation to a corresponding parameter in a blue box below it:

- A_v points to A_{Vo}
- f points to BW
- V_{in} points to THD
- R_L points to R_O
- R_S points to R_{IN}
- $\tilde{e}_N$ points to NF

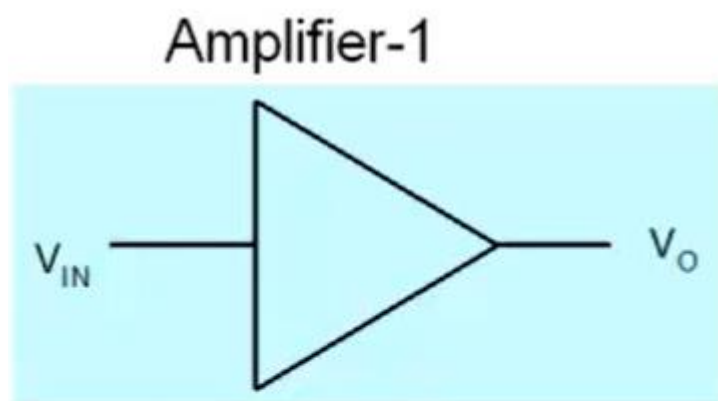
Create situations where one amplifier is better than the other



$$A_{V0} = 10^2$$

$$R_{in} = 1k\Omega$$

$$R_o = 1k\Omega$$

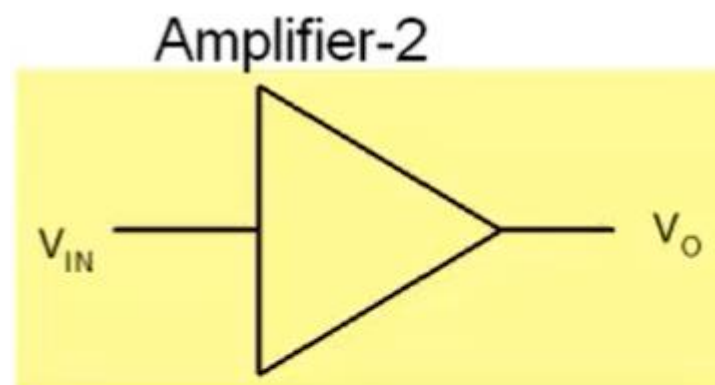

$$A_{V0} = 10^1$$

$$R_{in} = 100k\Omega$$

$$R_o = 1k\Omega$$

Can the following amplifier be useful?

Can it be called an amplifier?

$$A_{V0} = 1; R_{in} = 10k\Omega; R_o = 10\Omega$$

Semiconductor Basics: A quick review


Semiconductor Basics: A quick review

Energy Bands

- ① Energy levels in atom are discrete (1s, 2s, ---)
- ② In crystal → these levels broaden into Bands.


- ③ As these energy levels expand into bands, these energy levels also mix, therefore band structure becomes complicated.

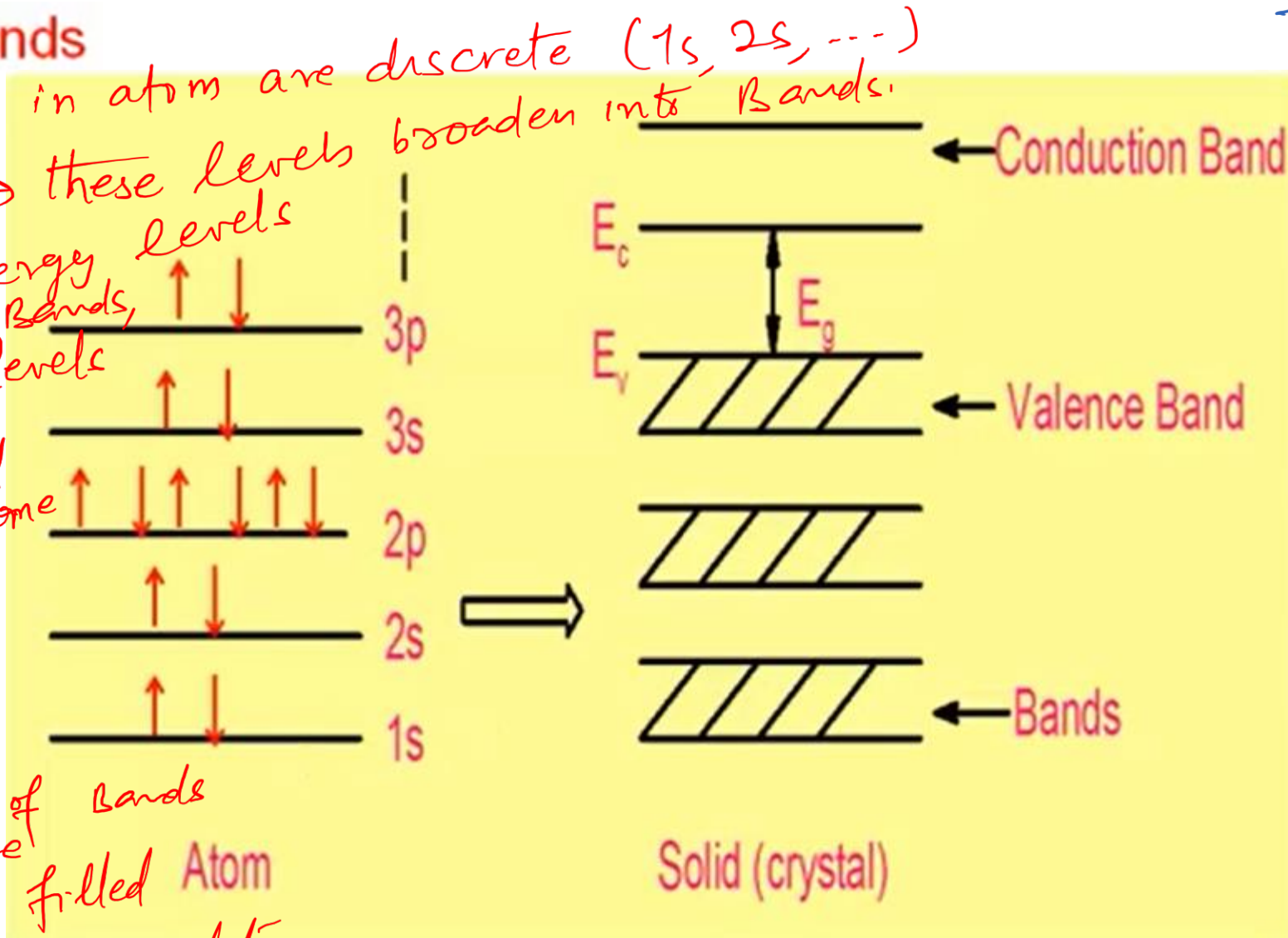- ④ Examine the band e.g., (Si) have series of bands → some are completely filled i.e., can't accommodate more e




A completely full band of electrons cannot contribute to current conduction !

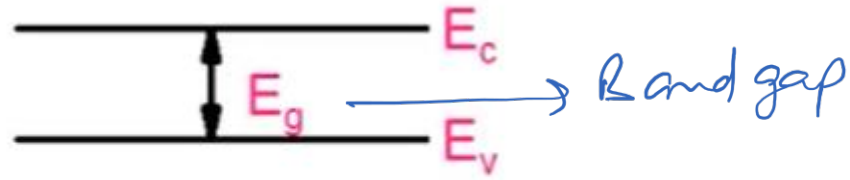- ⑤ But, in semiconductor,
 - some Bands are fully filled
 - some are empty
 - Nature of semiconductor at 0°C
 - Bands which are of interest in semiconductor are top most
 - Valence Band
 - Conduction Band.



- ① at room temperature
 • Some of e^- in VB, gain enough energy from thermal field $\rightarrow$ They are able to pass E_g
- $E_g = 1.12 \text{ eV}$ for Silicon at 0°K ($\approx -273^\circ\text{C}$)

Generation
of
Carrier $\leftarrow$

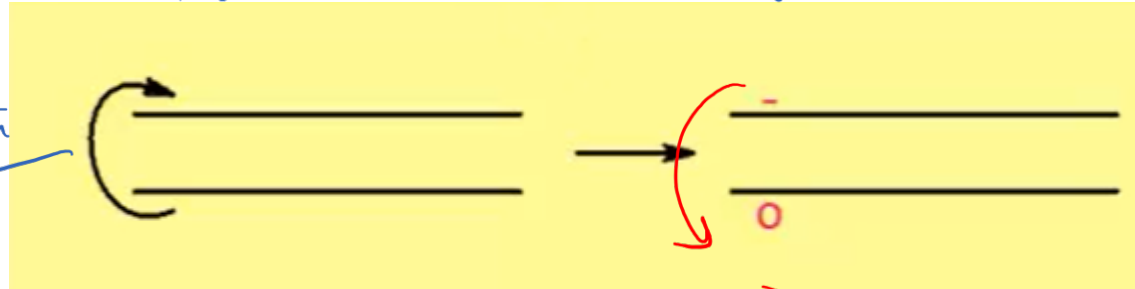

- ② Now, e^- are in CB, when applied $\vec{E}$, they may move and conduct current.


$$n = p = n_i$$

$$n_i = 1.45 \times 10^{10} \text{ cm}^{-3} \quad (T = 300\text{K})$$

$\rightarrow$ Recombination


- ③ In equilibrium:
 Generation and Recombination $\rightarrow$ Two processes balance each other
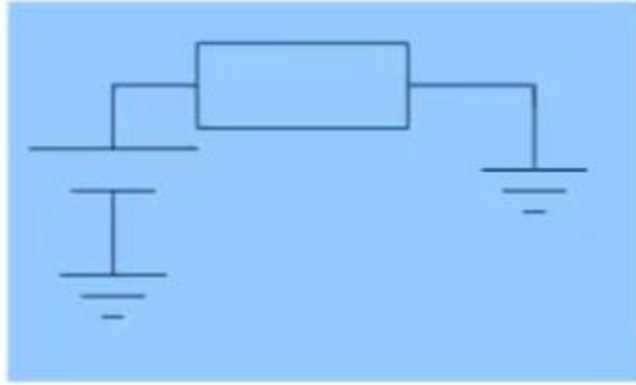
$$n_i \propto \exp\left(-\frac{E_g}{2kT}\right)$$



$$J = \sigma E$$
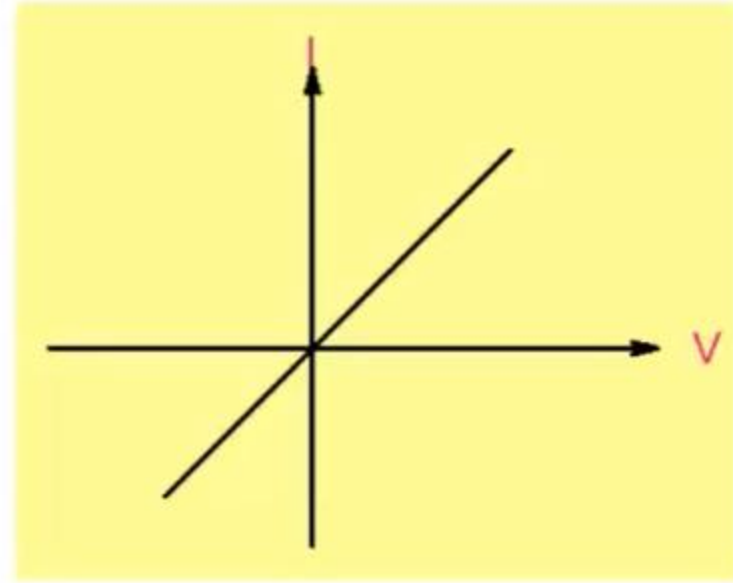
$$I = \frac{V}{R} ; R = \frac{1}{\sigma} \times \frac{L}{W}$$



conductivity

amount of $\bar{E}$ or h^+

$$\sigma_i = q(\mu_n + \mu_p)n_i$$


$$\sigma_i \approx 4 \times 10^{-6} \Omega^{-1} \text{ cm}^{-1}$$

$$\rho_i \approx 2 \times 10^5 \Omega \text{ cm}$$


pure semiconductor
is pretty resistive
→ current will be small

Doping

N-Type Semiconductor

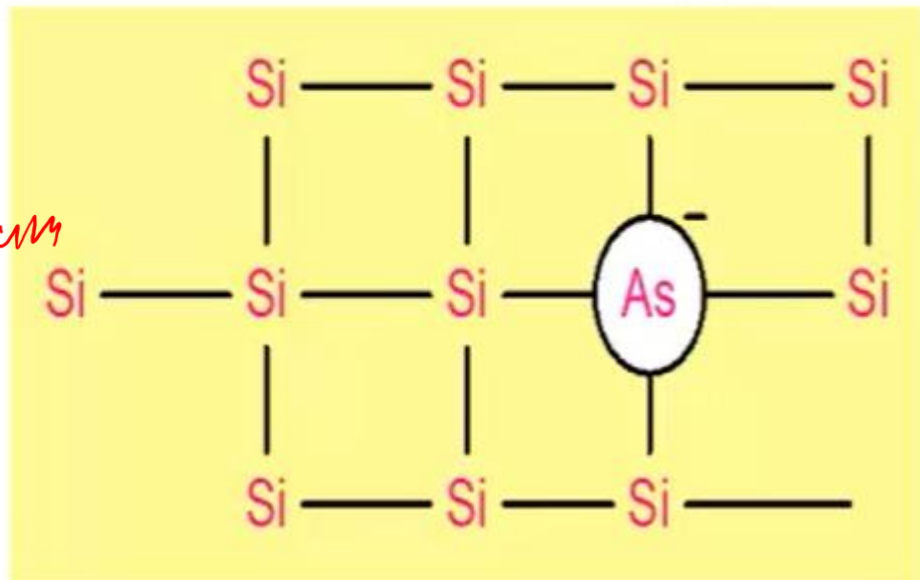

⑤ In equilibrium
 $n \cdot p = n_i^2$

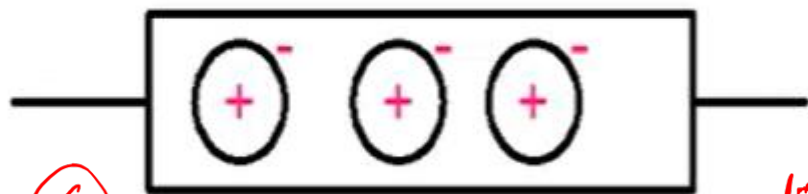


⑥ why no. of h^+ decreased?

• P, As, Sb, Bi $\rightarrow$ pentavalent (Donor) (V group)

① Extra $\bar{e}$ is loosely bound and it goes to CB.

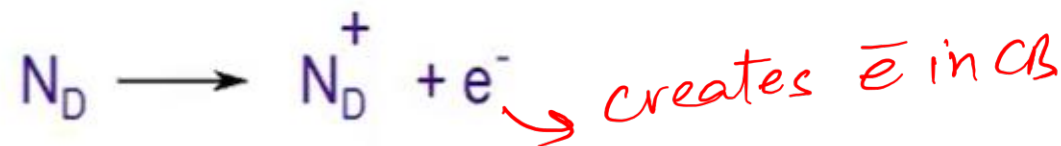② So, when we add (e.g., As); it adds extra $\bar{e}$ in CB.



③ In this process $\rightarrow h^+$ are not created.

• Source of $\bar{e}$ is Donor atom, it gets ionized become positively charged and creates an $\bar{e}$ in CB.

$$N_D = 10^{16} \text{ cm}^{-3}$$

$$n \approx 10^{16} \text{ cm}^{-3}$$

$$p \approx n_i^2 / n \approx 2 \times 10^4 \text{ cm}^{-3}$$

$$n \gg p$$

④ Normally, donor atom is large, positively charged, it can't move
 $\downarrow$
 immobile

Small amount of impurity results in large change in resistivity !

No. of carrier
↓

$$\sigma_i = q(\mu_n + \mu_p) n_i$$

• σ depend on n_i

No. of Silicon atoms / volume = $5 \times 10^{22} \text{ cm}^{-3}$

$$\frac{10^{16}}{5 \times 10^{22}} = 2 \times 10^{-7} \quad (0.2 \text{ PPM})$$


now → 10^{16}
↓

$$\rho : 2 \times 10^5 \, \Omega \text{ cm} \xrightarrow{N_D = 10^{16} \text{ cm}^{-3}} \underline{1.5 \, \Omega \text{ cm}}$$

unique property in semiconductor

P-Type Semiconductor

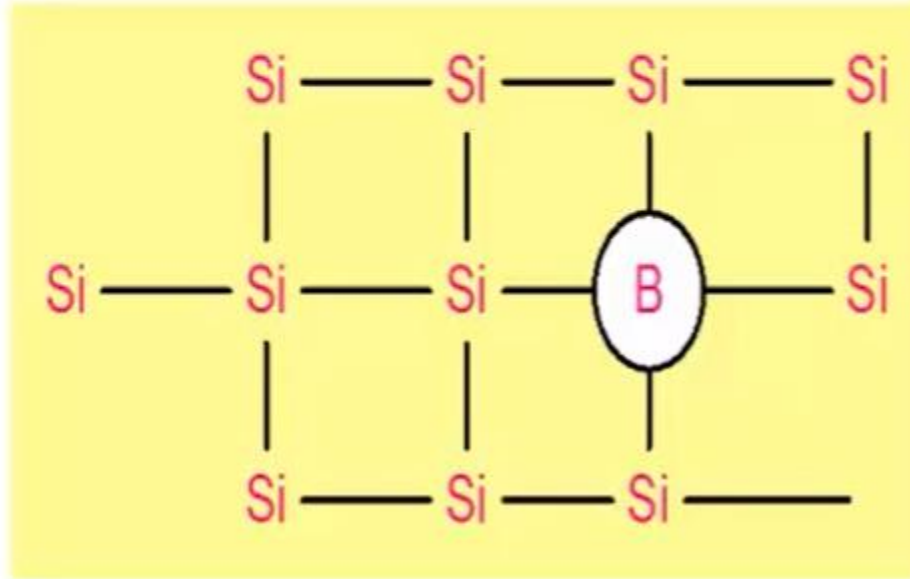B, Al, Ga $\rightarrow$ Trivalent impurity



$\rightarrow$ creates h^+ in VB

$$N_A = 10^{16} \text{ cm}^{-3}$$

$$p \approx 10^{16} \text{ cm}^{-3}$$

$$n \approx n_i^2 / p = 2 \times 10^4 \text{ cm}^{-3}$$


$$p \gg n$$

Number of carriers is dependent on temperature !

- ① $\bar{e}$ come from the Donor atom (As).
• It is attached to donor atom
- ② when we go to very low temp

↓
 $\bar{e}$ doesn't have enough energy to go to CB.
 • It stays bond to "As" atom

↓
 Donor freezeout

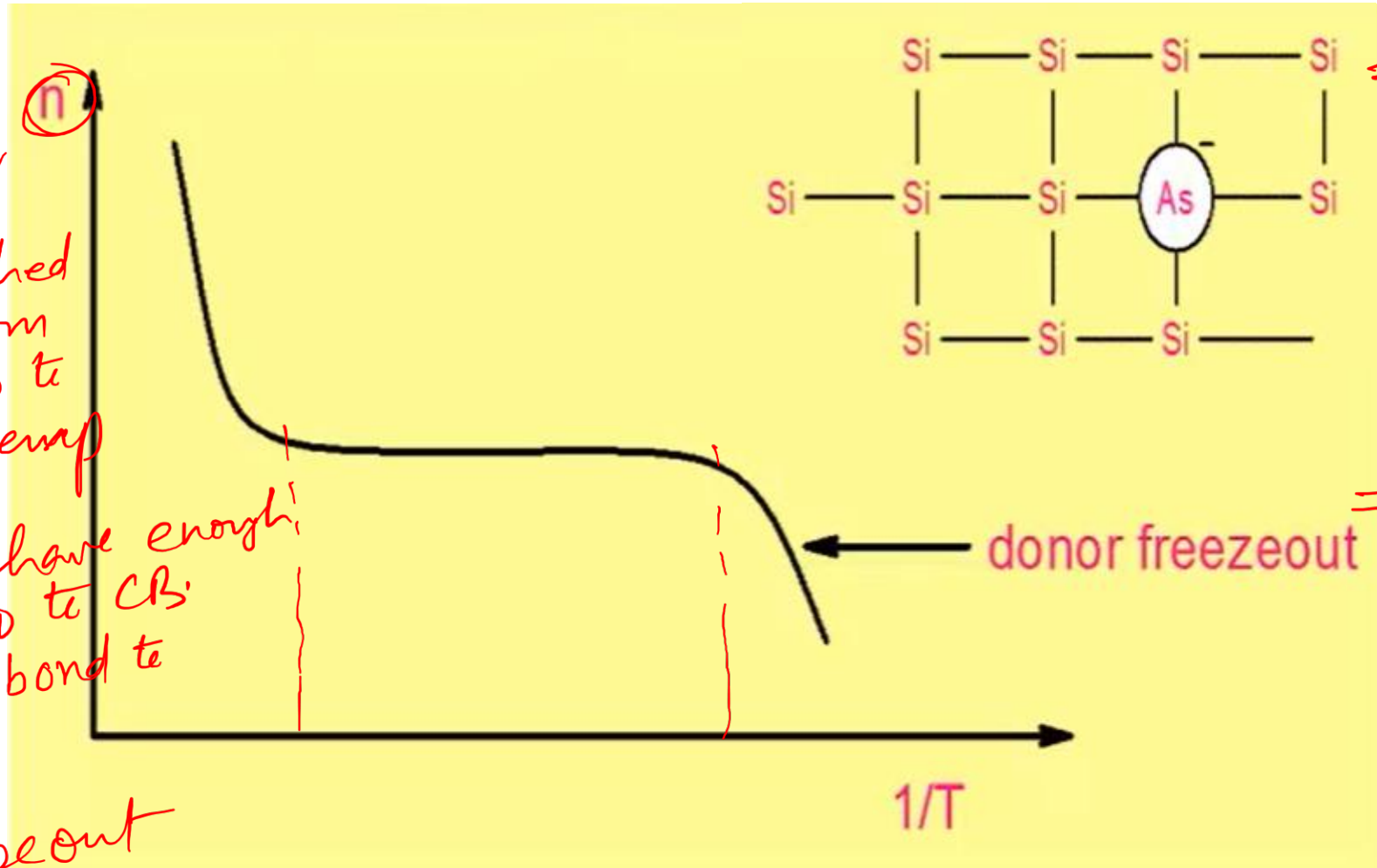

③ At High temp:

$$\Rightarrow n \propto \exp\left(\frac{-E_g}{2KT}\right)$$

• what are sources of $\bar{e}$


↓ Thermal Energy ↓ Doping

⇒ Now, Temp ↑
 Thermally created $\bar{e}$ and h^+ are comparable
 e.g. 10^{16}

→ material become intrinsic

Current flow

Drift due to Electric field

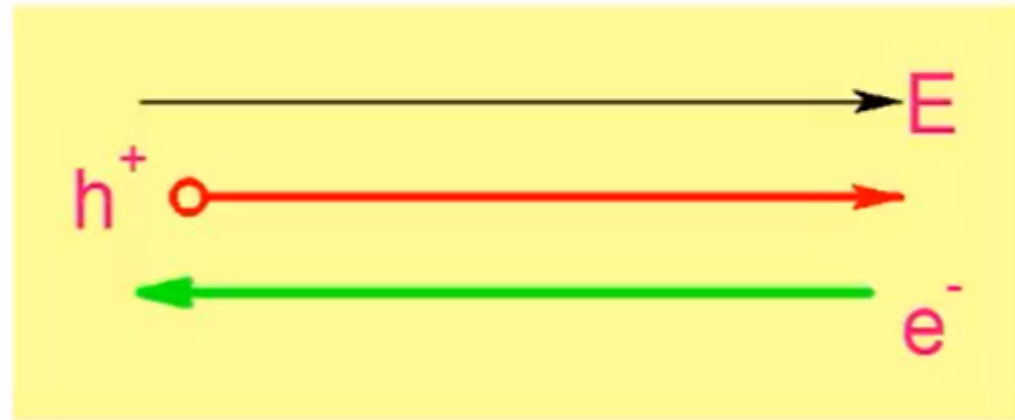

Current
Density $\rightarrow$

$$J_n = qn\mu_n E$$


$$J_p = qp\mu_p E$$

$$J = J_n + J_p$$

Current flow

[Even when no electric field]

Diffusion to concentration gradient

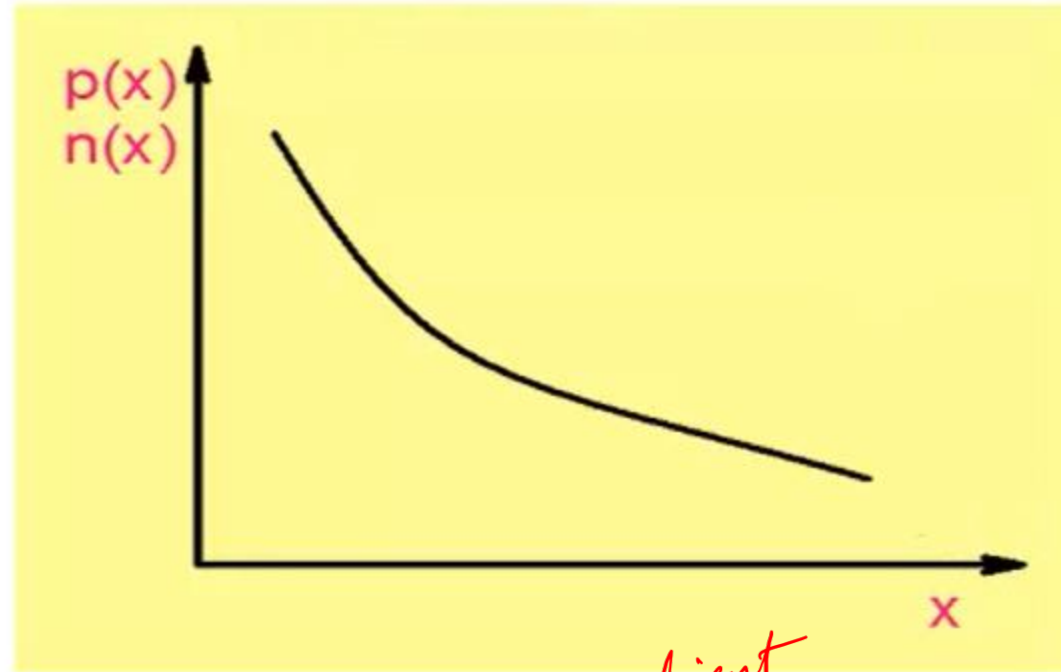

→ Gradient


$$J_n = qD_n \frac{\partial n}{\partial x}$$

$$J_p = -qD_p \frac{\partial p}{\partial x}$$




↓
Diffusion
coeff



PN Junction Diode

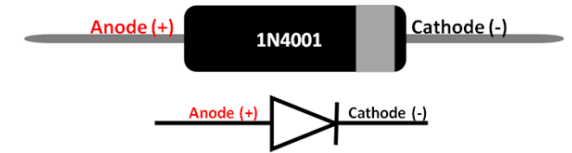


PN Junction Diode

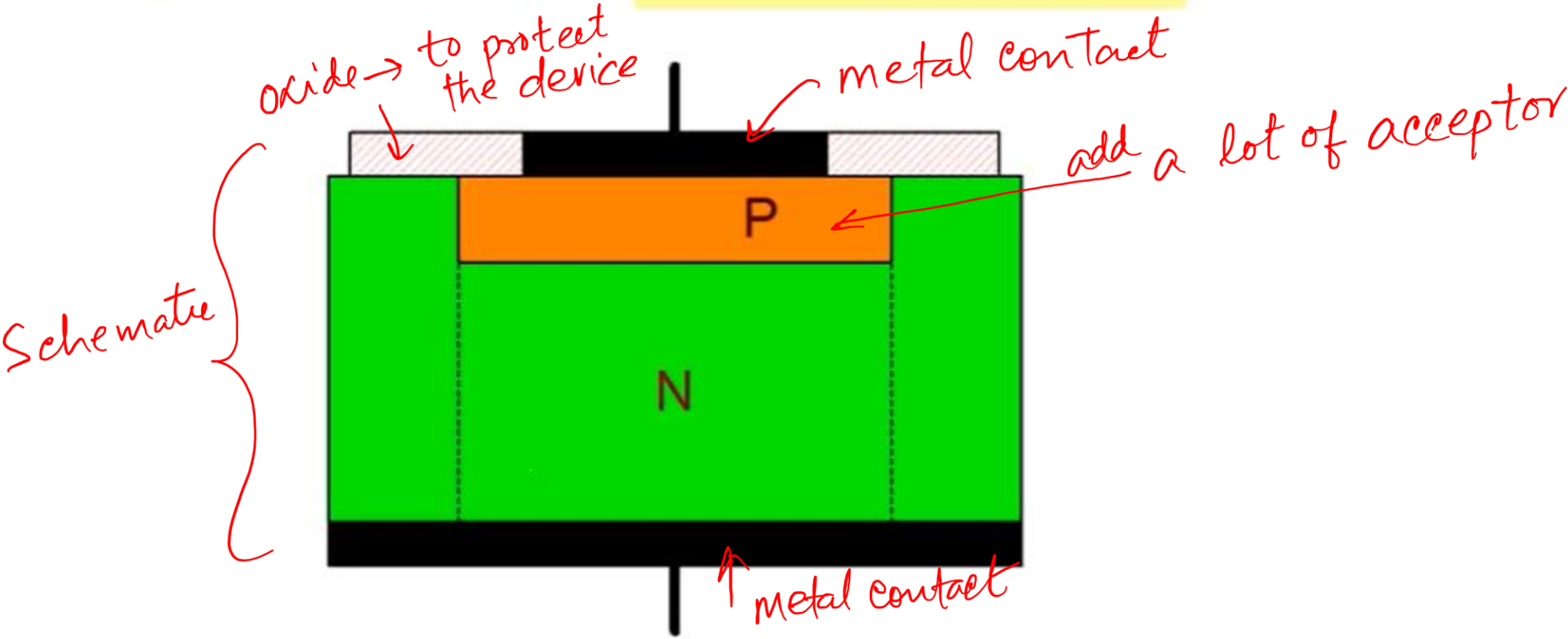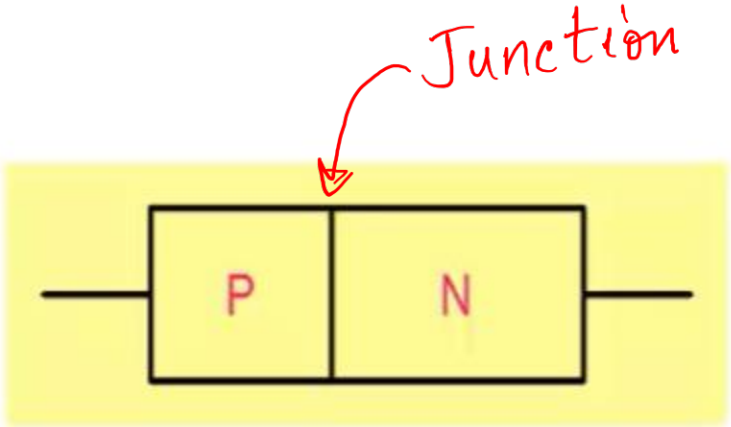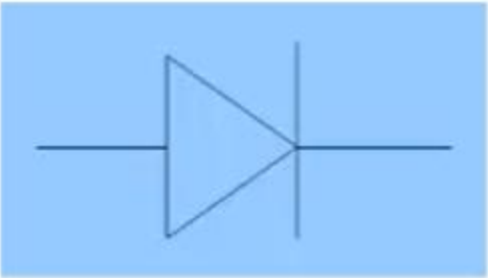


Basic Operation

$$N_i^2 = 10^{20}$$

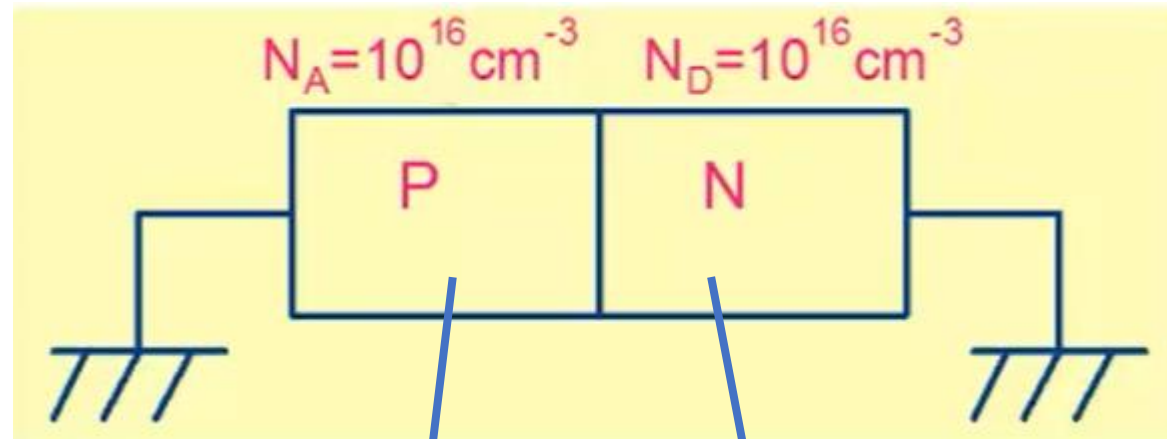


acceptor
impurity
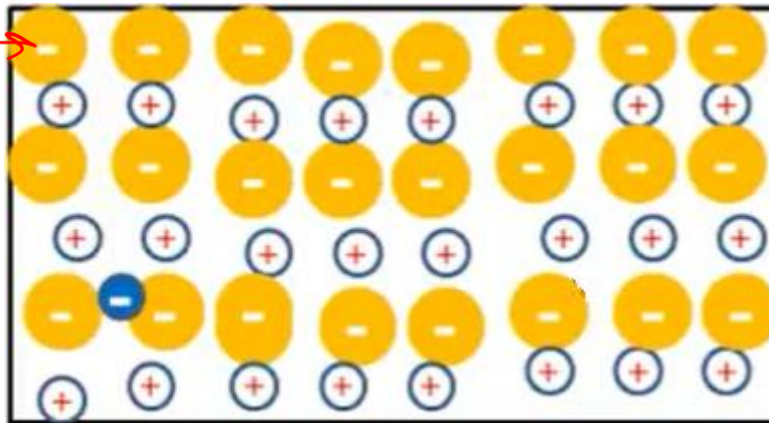
$$p = 10^{16} \text{ cm}^{-3} ; n \sim 10^4 \text{ cm}^{-3}$$


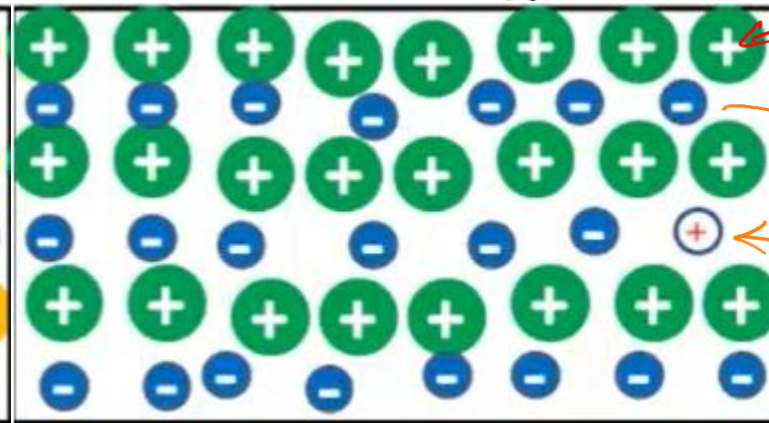
$$n = 10^{16} \text{ cm}^{-3} ; p \sim 10^4 \text{ cm}^{-3}$$



Donor
impurity

electron (e^-)

Hole (h^+)

Holes will tend to diffuse from p $\rightarrow$ n and electrons from n $\rightarrow$ p

④ when $\bar{e}$ move to p-side $\rightarrow$ it finds a sea of holes $\rightarrow$ Holes are empty states $\rightarrow \bar{e}$ fall into it

⑤ We can see it what happened;

This $\bar{e}$ was covering this positive charge i.e., neutralizing it.

Now $\bar{e}$ is not there to neutralize it.




• so, this local region become positive charge on n-side

• on the p-side, the local region become negative charge.



① what are two processes which cause a carrier to move
 $\swarrow$ Drift
 $\searrow$ Diffusion

② We have huge gradient e.g., a lot of $\bar{e}$ on n-side and a very few on p-type.

③ Similarly, a huge gradient for holes

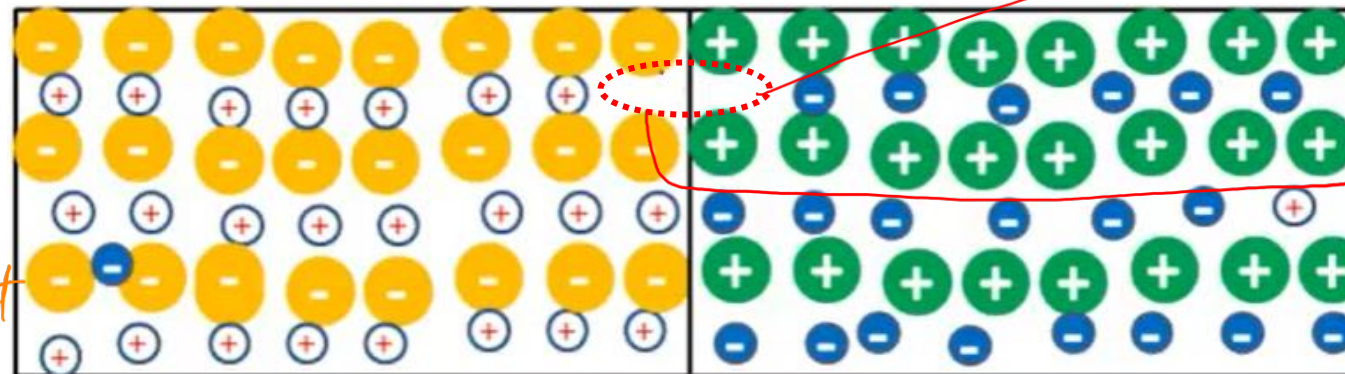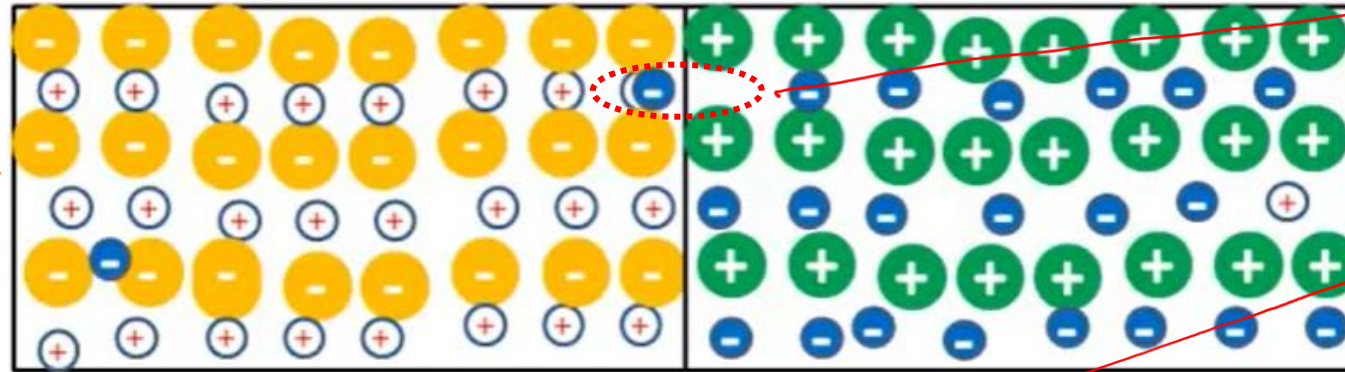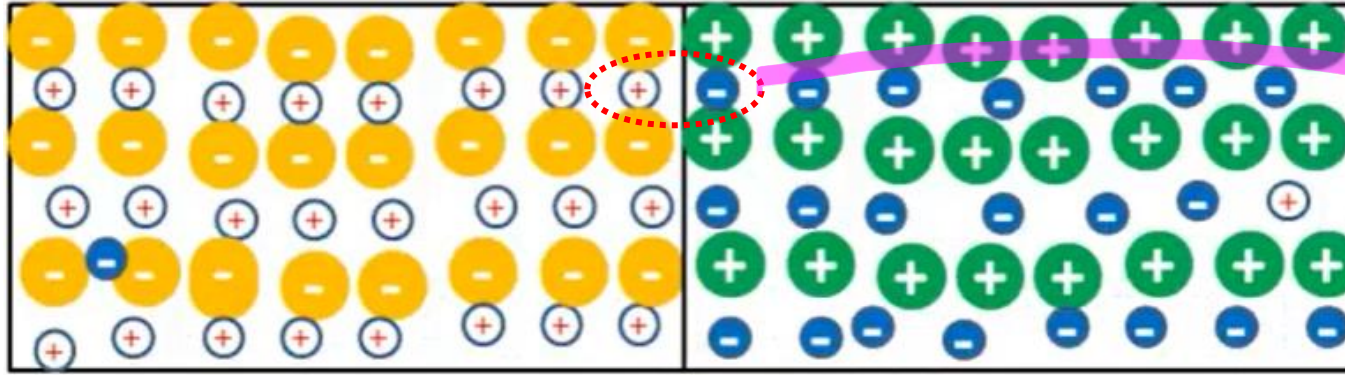


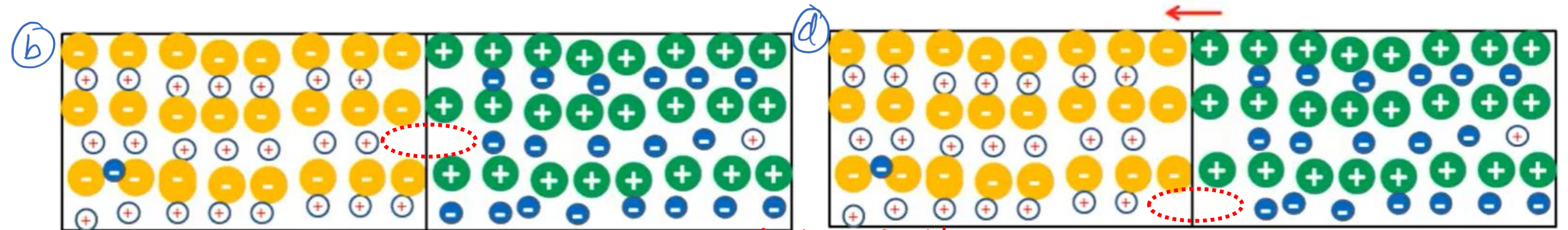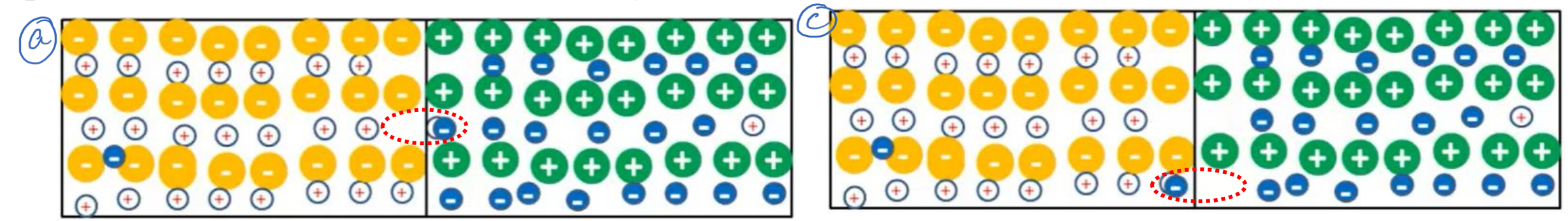① h^+ also go over to n-side $\rightarrow h^+$ finds a lot of e^- $\rightarrow$ ready to fall into it.



② Now, as a result of which $\rightarrow$ there is an electric field because we got an positive charge

Electric field opposes flow of carriers

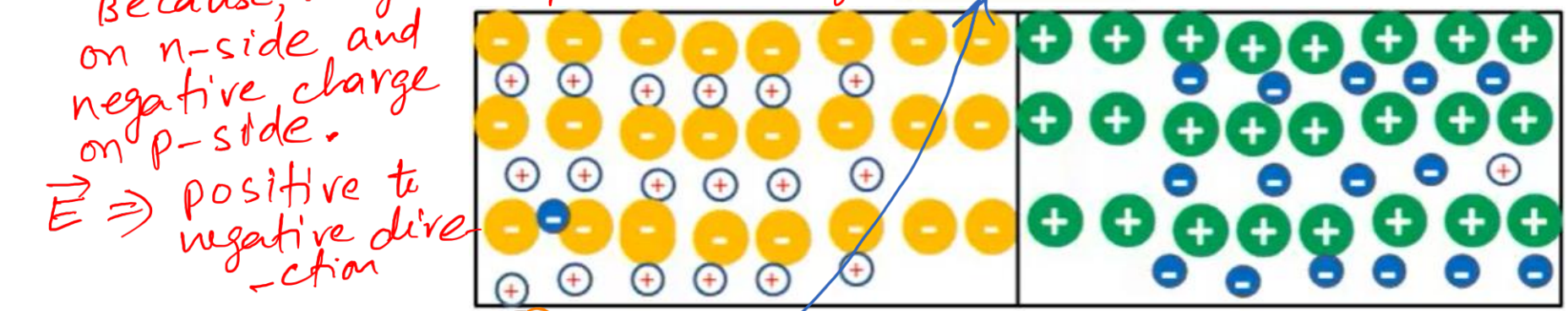

- ③ what this field will do?
- This field will prevent moving h^+ (note the direction of E)
 - This field will oppose the movement of the h^+
 - Now h^+ and e^- will find a little difficulty in movement.
 - still, our Diffusion gradient is very high.
 - So, the process will continue


④ Now, what happens? ⑤ Eventually equilibrium is reached and there is no net flow of carriers across the junction

PN Junction Under Equilibrium

① when we reached equilibrium → what will be find?
 • a region close to junction has lost carrier

Although small, depletion region has some carriers

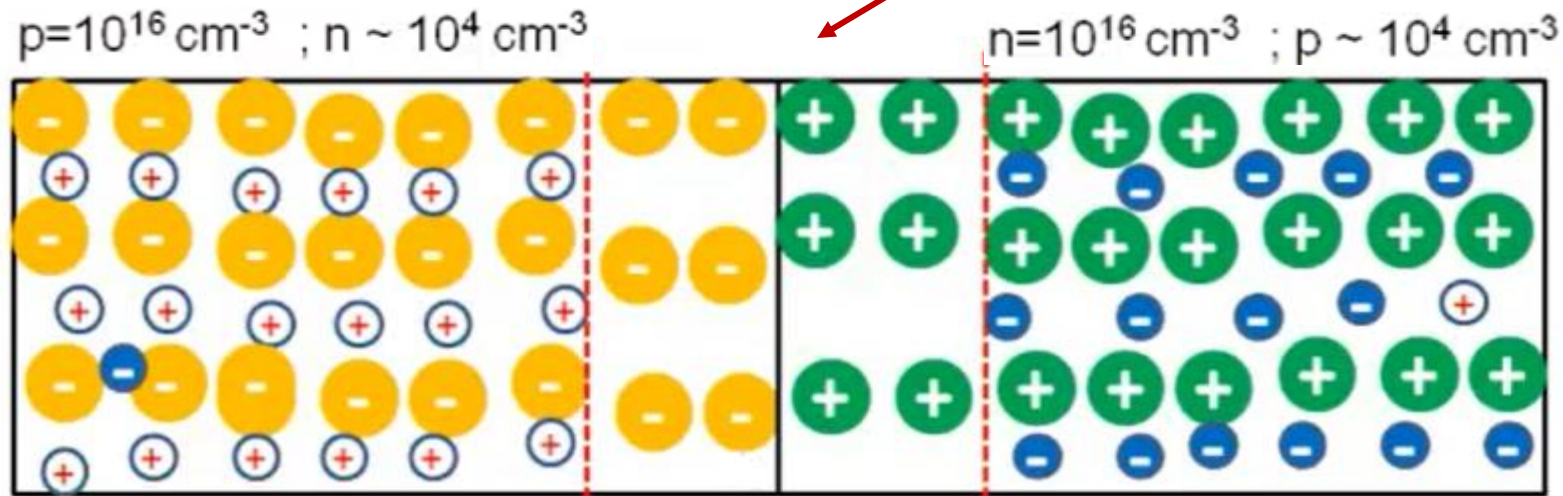Note: It is not like, this region has completely devoid of carrier → But has lost some carriers




Space charge region
Depletion region

neutral

→ $N_D \gg n$

• That is why we call this region as positive charge.
 • e^- are not able to neutralize the donors

Depletion region

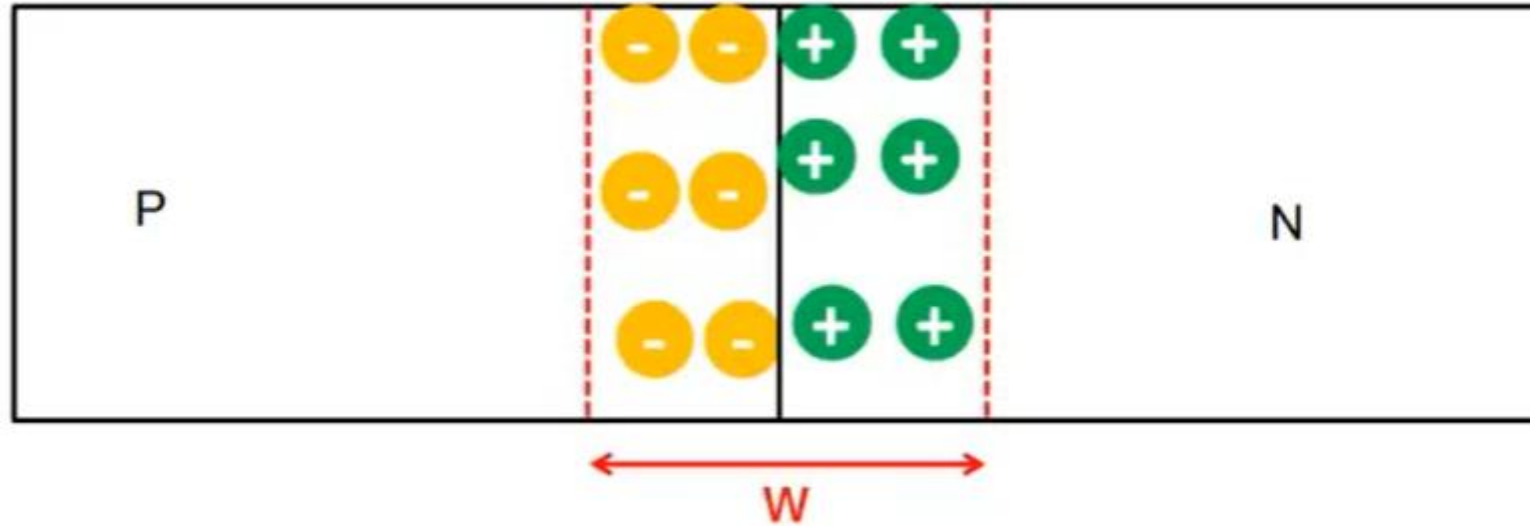

$$W = \sqrt{\frac{2\epsilon_s}{q} \times \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \times V_{bi}}$$

$$\epsilon_s = 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}; q = 1.6 \times 10^{-19} \text{ C}$$

$$N_A = N_D = 10^{16} \text{ cm}^{-3}, T = 300^\circ\text{K}$$


$$V_{bi} = 0.86 \text{ V}$$

$$W = 4300 \text{ \AA}$$

order is like $2000 \text{ \AA}$
or $3000 \text{ \AA}$, etc

Built-in Potential V_{bi}

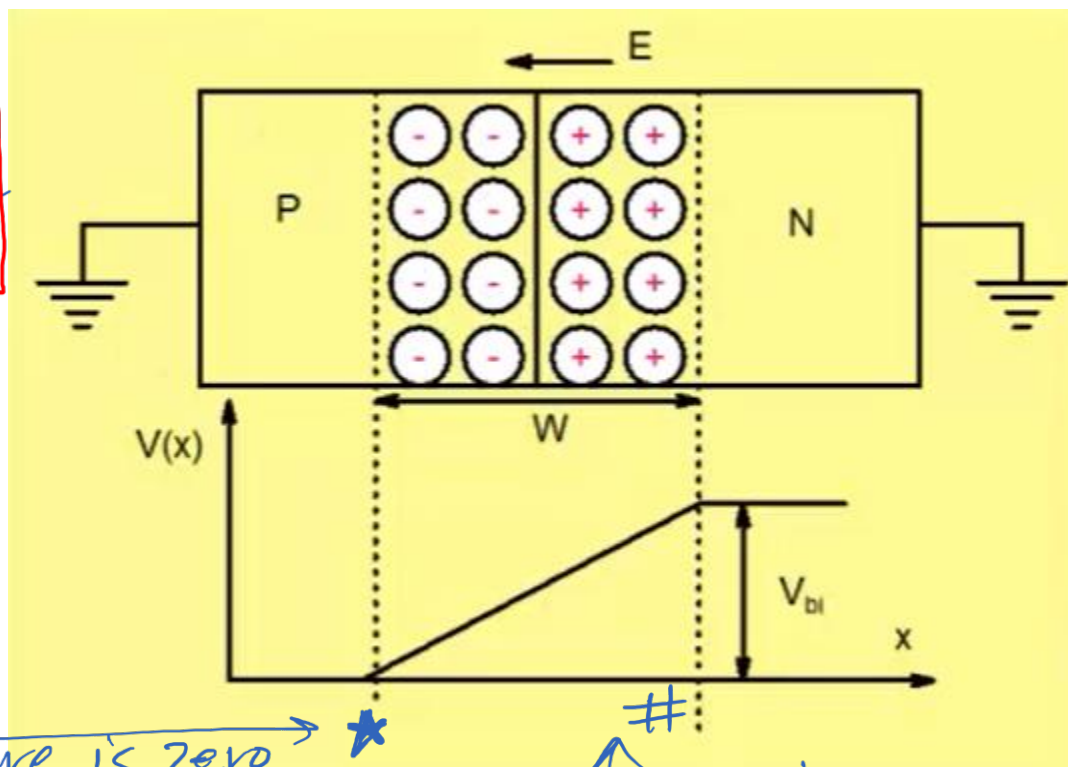- ① once equilibrium is reached $\rightarrow$ we have depletion region
- ② In depletion region $\rightarrow$ we have $\vec{E}$ (look at the direction)



- ④ From eqⁿ (A)
 - V_{bi} depends on doping but not very sensitive to doping
 - $\rightarrow$ log of doping

③

- If we assume that potential here is zero $\rightarrow$ *
- what will be potential here $\rightarrow$ something higher

$$V_{bi} = \frac{kT}{q} \ln \left[\frac{N_A N_D}{n_i^2} \right]$$

$$N_A = N_D = 10^{16} \text{ cm}^{-3}, T = 300^\circ \text{K}$$

$$V_{bi} = 0.86 \text{ V}$$


Notice: Anytime you put two different materials into contact, a potential develops between them. $\rightarrow$ we call this Built-in potential.

Note: It is not something we have applied externally. It is part of our PN-junction.


• let's look at broader picture

Built-in Potential

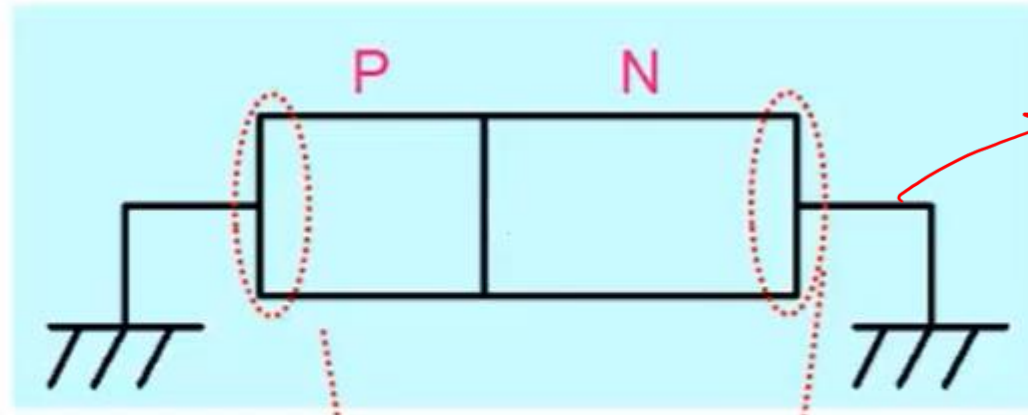• You will not be able to measure Built-in potential in multimeter.



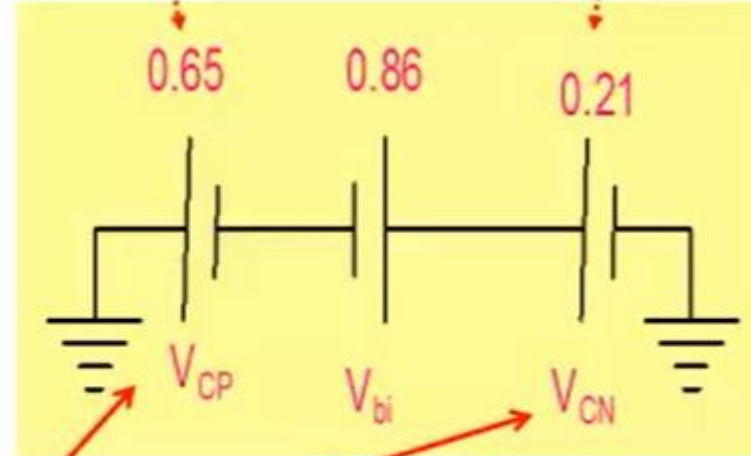① copper wire
• we have a contact potential between n-type and a copper wire



Contact potential

• contacts are transparent to carriers
↓
ohmic

• The Behaviour of pn-junction is determined by pn-jn contact.